

Addressing Conceptual Difficulties in Electrical Circuits: What is V? What is I? What is R?

A. John Mallinckrodt

Physics Departments

Cal Poly Pomona
Pomona, CA 91768

and (1993-94)

Harvey Mudd College
Claremont, CA 91711

?

?

?

Outline

Survey of the literature:

- A typical response and an interpretation
- A catalog of common misconceptions

Working hypothesis:

- Conceptual difficulties are linked to inadequate or missing **qualitative** models connecting macroscopic observations with microscopic interactions.


Elements of a **qualitative, concept-oriented** approach

- Proper use of words and symbols
- Macro/Micro viewpoints
- Magnifying and exploiting transients
- A modified hydraulic analogy
- Resistance versus conductance
- Connecting wires as electrical points
- 3-D circuit diagrams
- Explicit comparison of current vs. emf sources
- Kirchhoff's rules and self-consistency

Summary

A Typical Response and an Interpretation

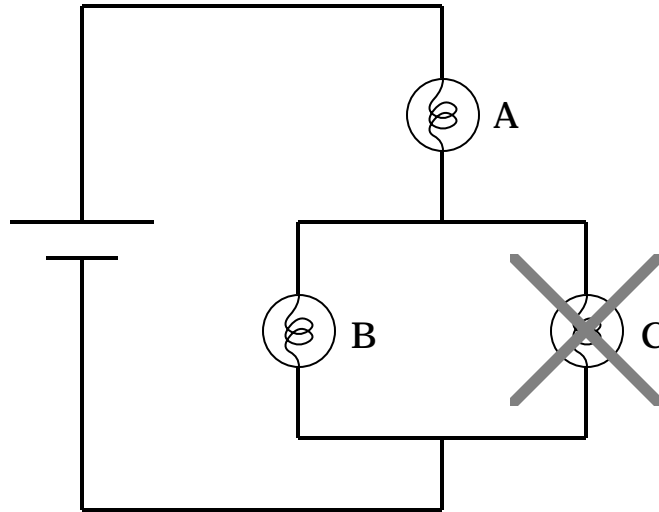Q: What happens to the brightness of bulbs A and B when bulb C is removed from this circuit



A: The current that used to flow through C must now pass through B. Therefore, B gets brighter. No change in A.

Interpretation: “Battery is constant current source” (?)

A Catalog of Common (Apparent) Misconceptions

- Batteries produce constant current.
- Charge/current originates in the battery.
- Charge/current is “used up” by circuit elements.
- Alterations in circuits have only “downstream” effects.
- Resistors (or light bulbs, etc.) are barriers to current flow; the more resistors the more resistance.
- Larger resistors use greater amounts of energy.
- Elements connected closer to the positive terminal (and thus “at higher voltage”) use larger amounts of energy.

Working Hypothesis

Conceptual difficulties are linked to inadequate or missing **qualitative** models connecting macroscopic observations with microscopic interactions.

This results in


- **undifferentiated views** of charge, current, potential, potential difference, energy, and power.
- lack of appreciation for the ways in which equilibrium is dictated by **self-consistency**.
- failure to recognize **global effects** of local changes.
- careless (or uncritically applied) language that reinforces (but also reveals) faulty concepts.

Words and Symbols

- Prepositions (e.g., “across,” “through,” “in,” “of,” ...)
- V (“potential,” not “voltage”) versus V (“potential difference” or “p.d.,” not “voltage”) $V = IR$ $V_B = V_A + V$
- Implications of the word “resistance.” How about “conductance”?
- Capacitance versus capacity
-
-
-

Macro-Micro Viewpoints

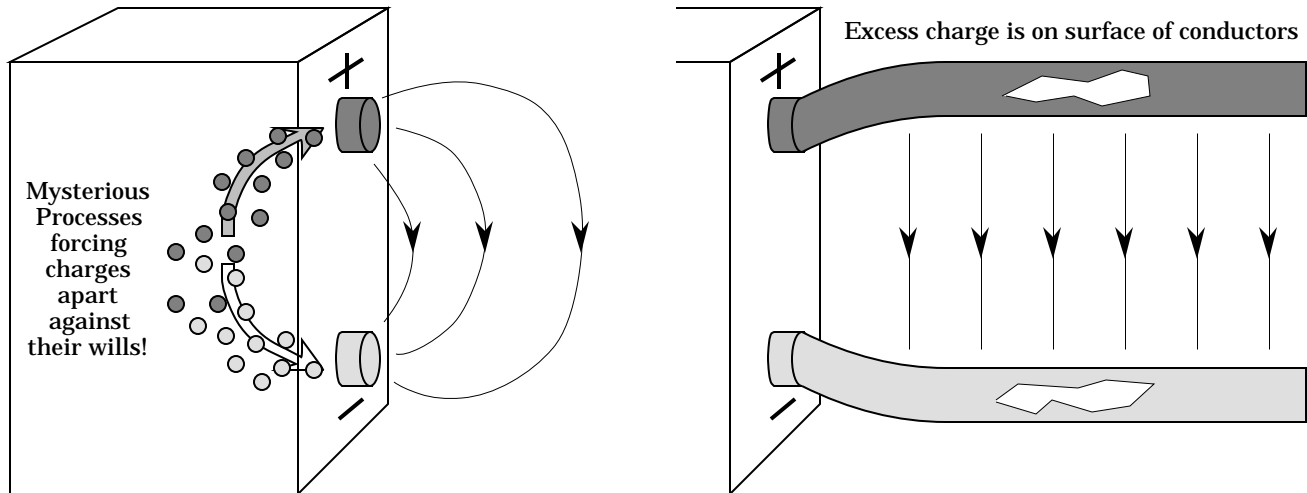- Batteries maintain a potential difference by separating charge.
- Potentials and electric fields in circuits are *the same kinds of things* and exist for *the same reasons* as in electrostatics.



Macro-Micro Viewpoint: Charge Arrangement


The “desired” steady state

- Excess charge on surface produces \mathbf{E} .
- \mathbf{E} drives steady (divergenceless) current.


Arriving at the steady state

- The arrangement takes time to establish.
- During the transient phase, current is *not* steady.
- Its divergence *produces* the excess charge.
- The excess charge appears just where it is needed.

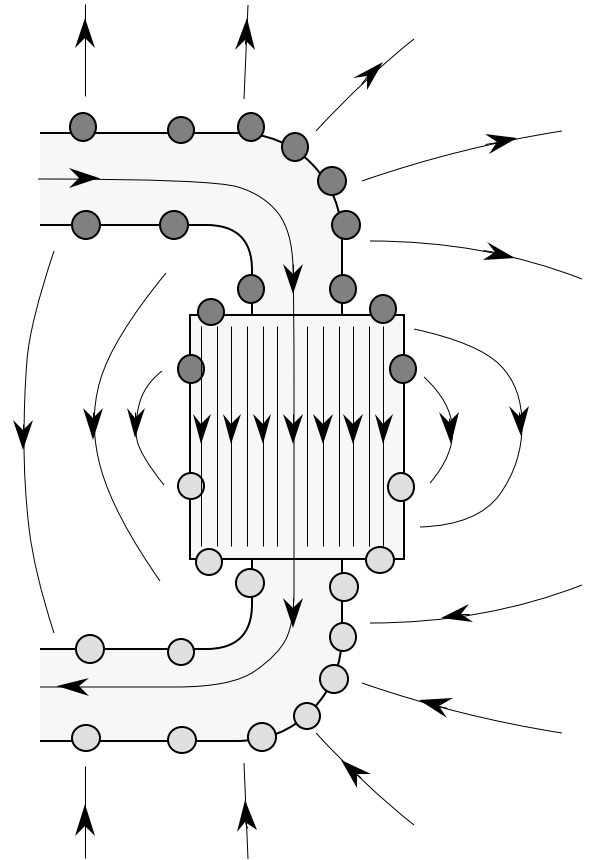
This process produces
and maintains a
self-consistent solution.



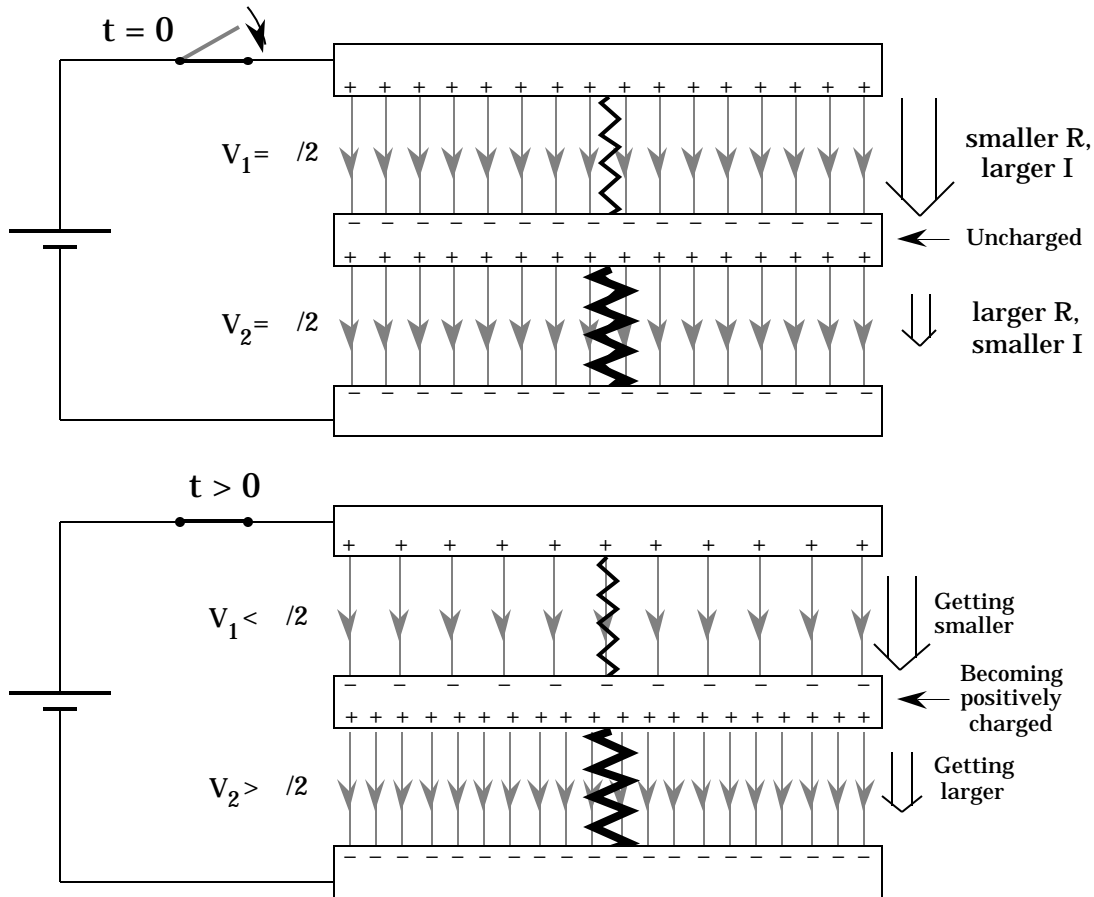Magnifying and Exploiting Transient Phenomena



Modified Hydraulic Analogy

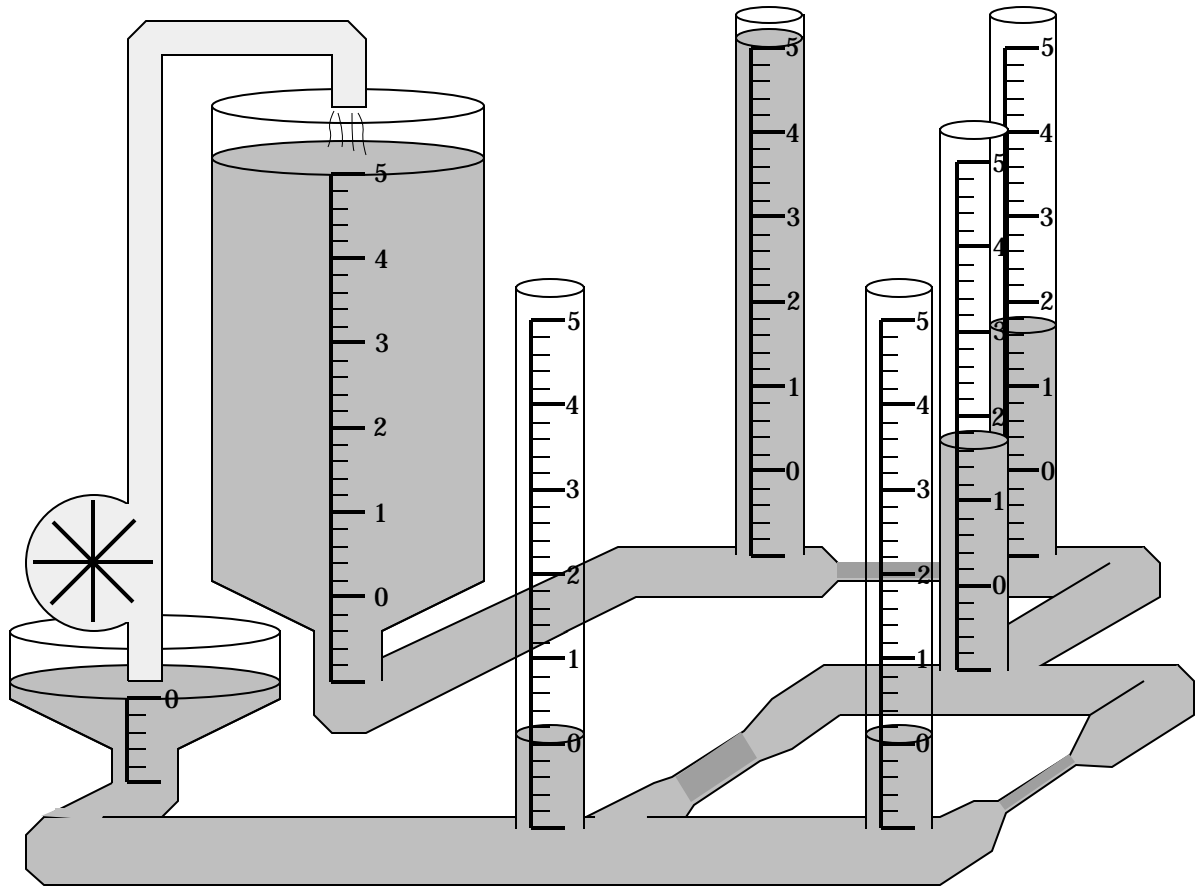


Is Resistance or Conductance the Relevant Concept?

- For elements in series, each element represents an additional *impediment* through which the current *must* flow.

“Resistance” is the appropriate concept.

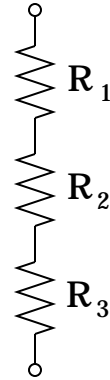
$$R_{\text{tot}} = R_1 + R_2 + R_3 + \dots$$






- For elements in parallel, each element represents an additional *path* through which current may *choose* to flow.

“Conductance” ($S = 1/R$) is the appropriate concept.

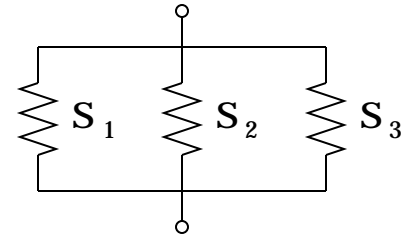
$$S_{\text{tot}} = S_1 + S_2 + S_3 + \dots$$



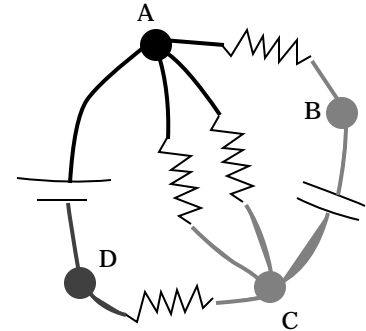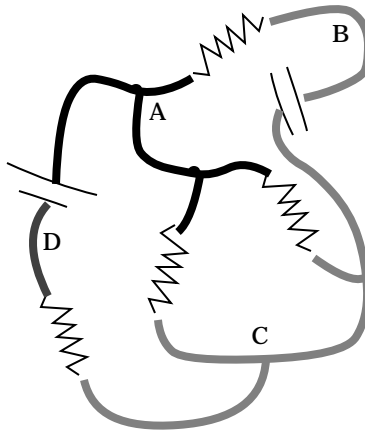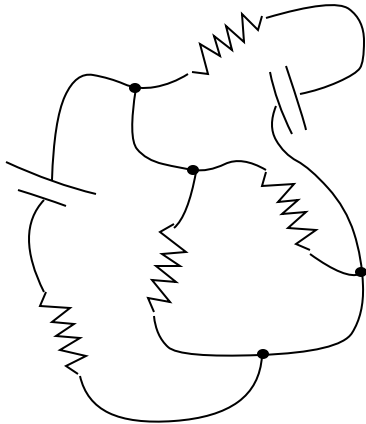
Deciphering Circuit Topology Using Electrical “Points”



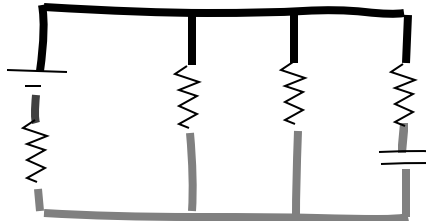
- Point A:** “Positive battery terminal is connected to three resistors.”
- Point B:** “One of these resistors is connected to a capacitor.”
- Point C:** “The capacitor and the other two resistors are connected to a fourth resistor.”
- Point D:** “The fourth resistor is connected to the negative battery terminal.”




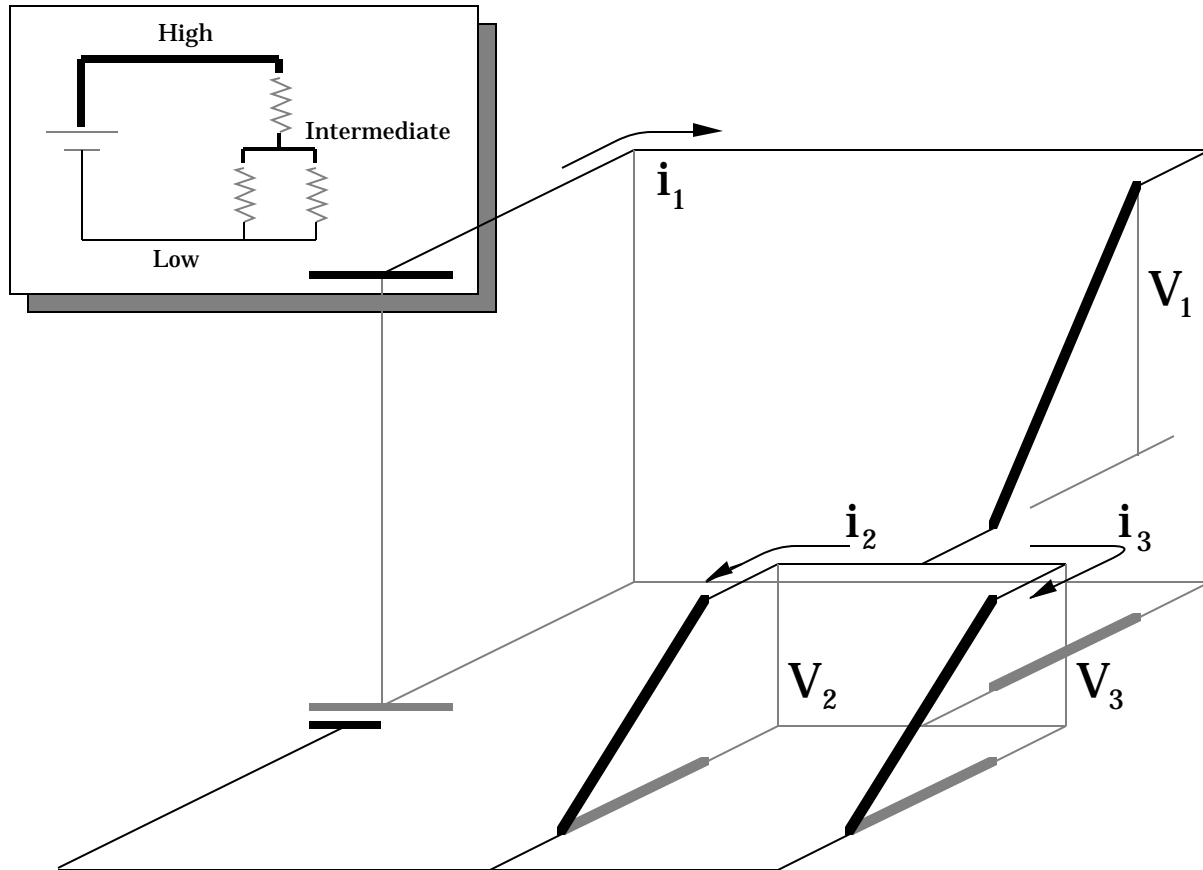3-D Diagrams for Visualizing Relative Potentials




What happens after the switch is closed?

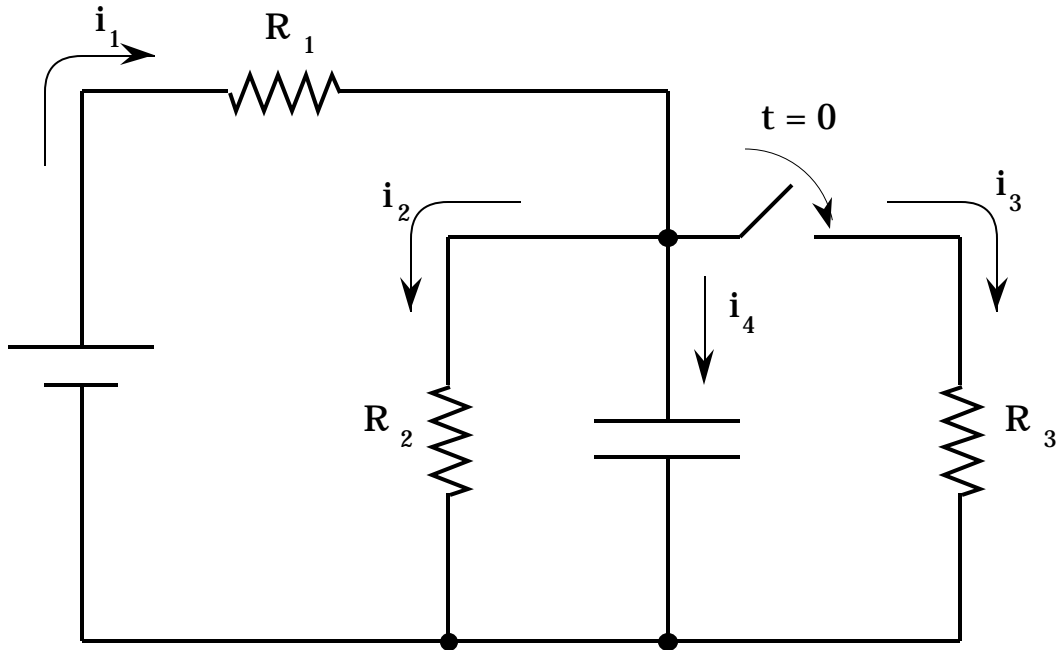

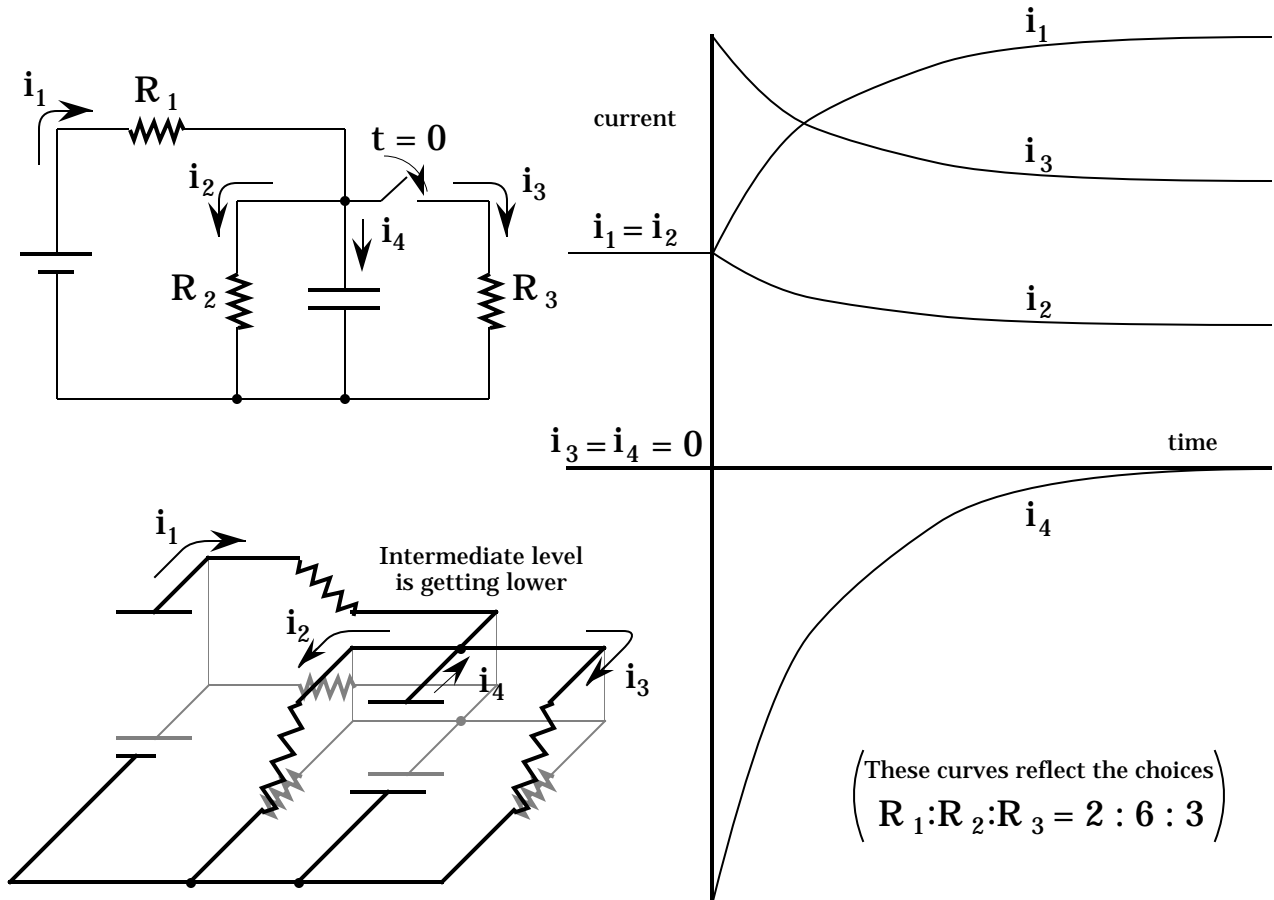


Removing a bulb: Constant current source

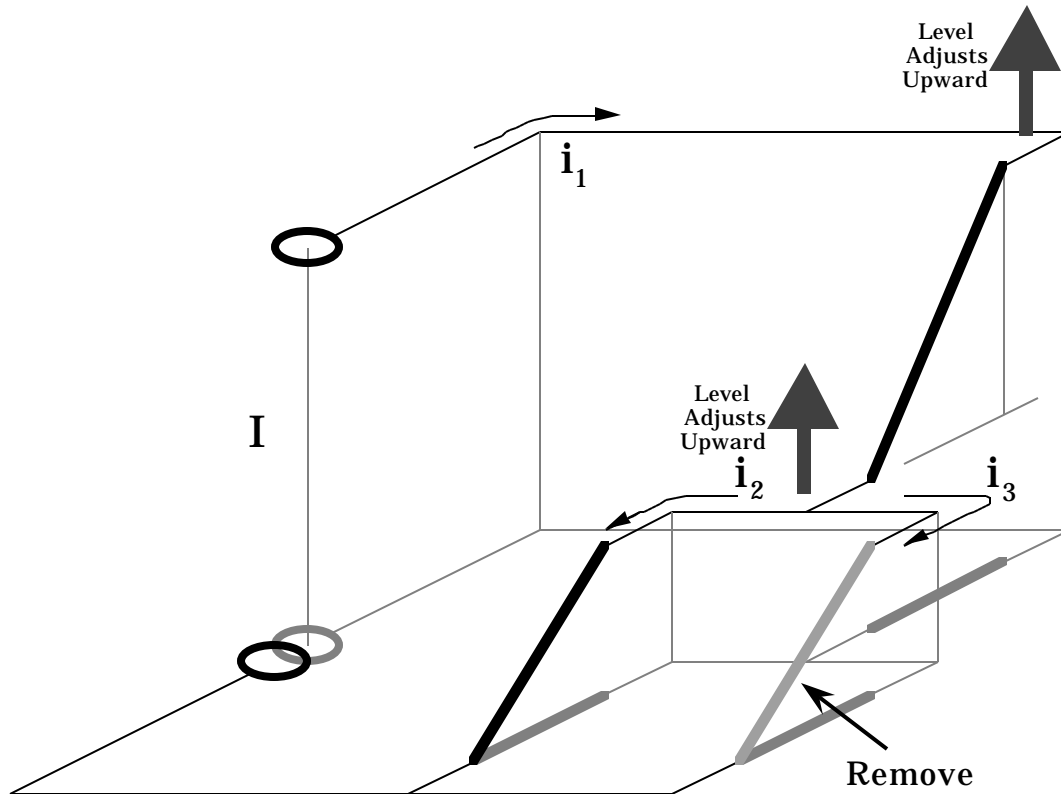

Before: $i_1 = I$, $i_2 = i_3 = I/2$

After: $i_1 = i_2 = I$ (#1 stays the same, #2 gets brighter)

Removing a bulb: Constant emf source

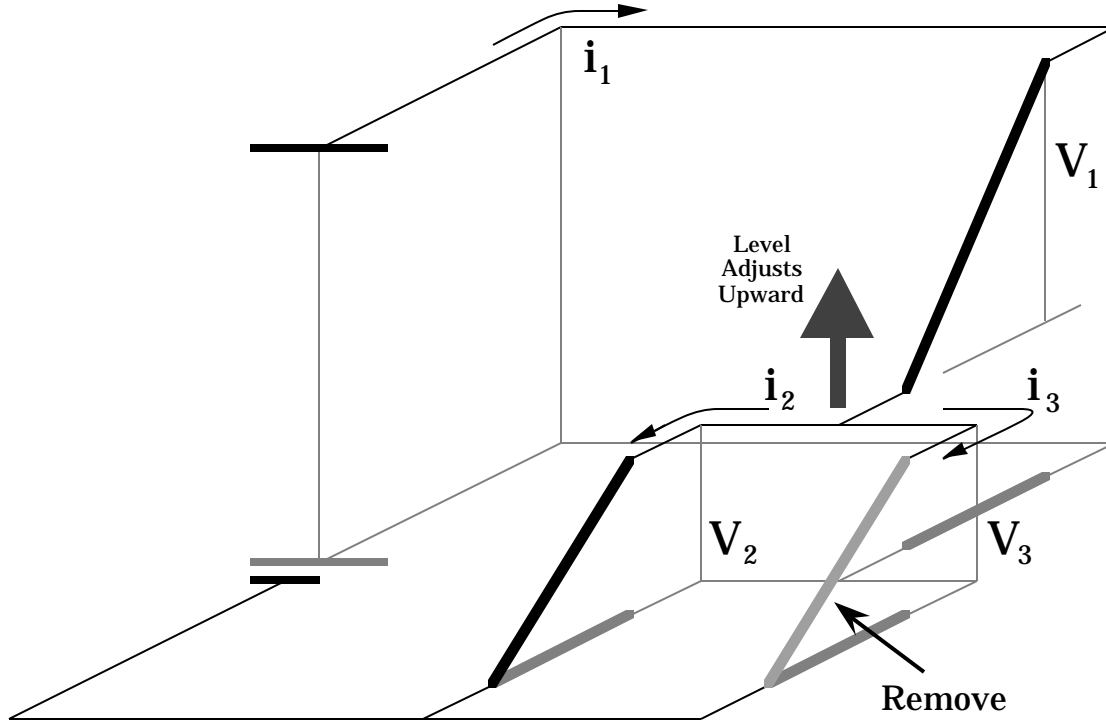


Before: $i_2 = i_3 = i_1/2$ $V_1 > V_2 = V_3$

After: $i_1 = i_2$ $V_1 = V_2 = V_3$ (#1 gets dimmer, #2 gets brighter)

Self-Consistency and Kirchhoff's Laws

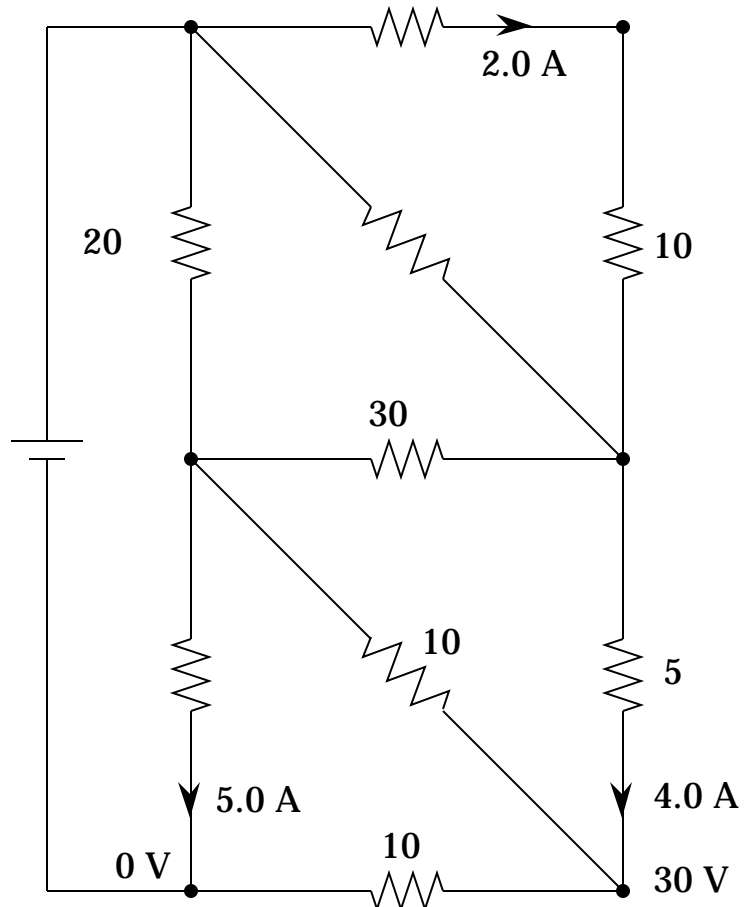- Six currents and four potentials to be determined.
- Five loops and five junctions yield ten Kirchhoff equations.
- Problem is designed so that a step-by-step method will work.



Summary

An old refrain:

An ability to solve traditional quantitative problems does *not* imply “understanding.”

Instructional approaches to electric circuits should include **qualitative, concept-oriented** material designed to enhance students’ ability to

- **differentiate** between charge, current, potential, potential difference, energy, and power.
- appreciate the ways in which equilibrium is dictated by **self-consistency**.
- recognize **global effects** of local changes.

Elements of such an approach

- Proper use of words and symbols
- Macro/Micro viewpoints
- Magnifying and exploiting transients
- A modified hydraulic analogy
- Resistance versus conductance
- Connecting wires as electrical points
- 3-D circuit diagrams
- Explicit comparison of current vs. emf sources
- Kirchoff’s rules and self-consistency

References

- J. Evans, "Teaching electricity with batteries and bulbs," *Phys. Teach.* **16**, 15 (1978).
- A.H. Johnstone and A.R. Mughol, "The concept of electrical resistance," *Phys. Educ.* **13**, 46 (1978).
- N. Fredette and J. Lochhead, "Student conceptions of simple circuits," *Phys. Teach.* **18**, 194 (1980).
- R. P. Bauman, "Hydraulic models for electrical circuit elements," *Phys. Teach.* **18**, 378 (1980).
- N. Fredette and J. Clement, "Student misconceptions of an electric circuit: What do they mean?" *J. Col. Sci. Teach.* **11**, 280 (1981).
- A.B. Arons, "Phenomenology and logical reasoning in introductory physics courses," *Am. J. Phys.* **50**, 13, (1982).
- R. Cohen, B. Eylon, and U. Ganiel, "Potential difference and current in simple electric circuits: A study of students' concepts," *Am. J. Phys.* **51**, 407 (1983).
- In *Misconceptions in Science and Mathematics—Proceedings of the International Seminar*, edited by H. Helm and J. D. Novak (Cornell U. P., Ithaca, NY 1983).
M. S. Steinberg, "Reinventing electricity"
- In *Aspects of Understanding Electricity—Proceedings of an International Workshop*, Ludwigsburg, Germany, edited by R. Duit, W. Jung, and C. v. Rhöneck (Verlag Schmidt & Klaunnig, Kiel, Germany, 1984).
L.C. McDermott and E. H. van Zee, "Identifying and addressing student difficulties with electric circuits"
D. M. Shipstone and R. F. Gunstone, "Teaching children to discriminate between current and energy"
M. S. Steinberg, "Construction of causal models: experimenting with capacitor-controlled transients as a means of promoting conceptual change"

- In *Misconceptions and Instructional Strategies in Science and Mathematics—Proceedings of the Second International Seminar*, edited by J. D. Novak (Cornell U. P., Ithaca, NY 1987).
 - M. S. Steinberg, “Transient electrical processes as resources for causal reasoning”
 - P. Licht, “A strategy to deal with conceptual and reasoning problems in introductory electricity education”
- M. S. Steinberg, “Transient lamp lighting with high-tech capacitors,” *Phys. Teach.* **25**, 95 (1987).
- D. Shipstone, “Pupils’ understanding of simple electrical circuits,” *Phys. Educ.* **23**, 92, (1988).
- P. Licht, “Teaching electrical energy, voltage and current: an alternative approach,” *Phys. Educ.* **26**, 272 (1991).
- L.C. McDermott and P. S. Shaffer, “Research as a guide for curriculum development: An example from introductory electricity. Part 1: Investigation of student understanding,” *Am. J. Phys.* **60**, 994 (1992).
- P. S. Shaffer and L.C. McDermott, “Research as a guide for curriculum development: An example from introductory electricity. Part II: Design of instructional strategies,” *Am. J. Phys.* **60**, 1003 (1992).
- P.M. Heller and F.N. Finley, “Variable uses of alternative conceptions: A case study in current electricity,” *J. Res. Sci. Teach.* **29**, 259, (1992).
- R. G. Newburgh, “Capacitors, water bottles, and Kirchhoff’s loop rule,” *Phys. Teach.* **31**, 16 (1993).
- R. A. Morse, “‘Feeling’ series and parallel resistances,” *Phys. Teach.* **31**, 347 (1993).
- M. S. Steinberg and C. L. Wainwright, “Using models to teach electricity—The CASTLE project,” *Phys. Teach.* **31**, 353 (1993).
- E. P. Mosca and M. L. De Jong, “Implications of using the CASTLE model,” *Phys. Teach.* **31**, 357 (1993).