

# ECE 306L - FOURIER SERIES - LAB 4


## HOW FILTERS AFFECT THE SPECTRUMS OF PULSE TRAINS

SPRING 2007

FELZER/KANG
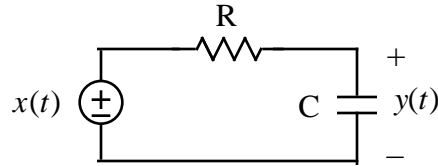
### OBJECTIVE


The objective of this lab is to see how the output  $y(t)$  of a lowpass filter like the following



depends on both the frequency response of the filter and spectrum of the input when  $x(t)$  is a pulse train

### PRELAB

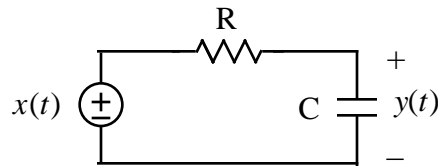
1. What do we mean by the frequency response of a linear circuit
2. The objective of this problem is to find the transfer function  $G(j2 f)$  of our first order RC circuit as follows



- a. Draw the phasor circuit
- b. Analyze your phasor circuit to show that its transfer function is equal to

$$G(j2 f) = \frac{1}{1 + j2 fRC}$$

3. Make use of Matlab to obtain a *full page* plot of the magnitude of the transfer function  $G(j2 f)$  with  $|G(j2 f)|$  plotted on a **linear scale** and  $f$  plotted on a **log scale**
4. Now suppose the input  $x(t)$  of our RC circuit with  $R = 10K$  is a 1/2 duty cycle pulse train as follows

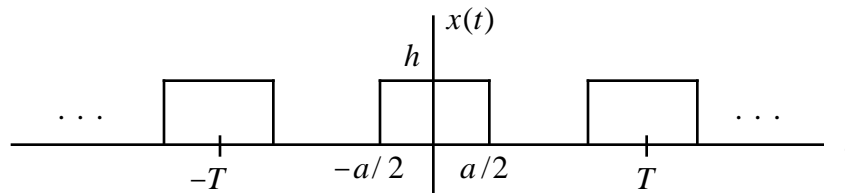

of amplitude  $h = 2$  and period  $T = 1$  msec

- a. Find  $C$  so that the RC time constant  $\tau$  is related to the pulse width  $a$  by  $a = 5\tau$
- b. Sketch what you expect the circuit's response to the pulse train looks like

- c. Use time domain arguments involving  $\tau$  to explain your graph in part (b)
- d. Use Matlab to plot the magnitude of the envelope  $X_{env}(f)$  with a dashed line
- e. Draw in the spectral lines by hand
- f. Use Matlab to plot the magnitude of the envelope  $Y_{env}(f)$  as follows with a dashed line

$$|Y_{env}(f)| = |X_{env}(f)||G(jf)|$$

- g. Draw in by hand the spectral lines for  $y(t)$
  - h. Compare the amplitudes of the spectral lines of  $x(t)$  and  $y(t)$
  - i. Make use of your result in part (h) to explain why  $x(t)$  and  $y(t)$  look so much alike
  - j. Use Matlab to obtain the magnitudes in dBV of the first ten spectral lines of the one-sided spectral plot of  $y(t)$
5. Again suppose  $x(t)$  is a 1/2 duty cycle pulse train of amplitude  $h = 2$  and period  $T = 1$  msec but this time suppose that the RC time constant  $\tau$  is related the pulse width  $a$  by  $a = 2\tau$
- a. Find  $C$  so that  $a = 2\tau$
  - b. Sketch what you expect the circuit's response to the pulse train looks like
  - c. Use time domain arguments involving  $\tau$  to explain your graph in part (b)
  - d. Use Matlab to plot the magnitude of the envelope  $Y_{env}(f)$  as follows with a dashed line

$$|Y_{env}(f)| = |X_{env}(f)||G(jf)|$$

- e. Draw in by hand the spectral lines for  $y(t)$
  - f. Compare the amplitudes of the spectral lines of  $x(t)$  and  $y(t)$
  - g. Make use of your result in part (f) to explain why  $x(t)$  and  $y(t)$  look different
  - h. Use Matlab to obtain the magnitudes in dBV of the first ten spectral lines of the one-sided spectral plot of  $y(t)$
6. Now suppose the RC circuit is the same as in Problem (4) but now the pulse train is 1/4 duty cycle with  $h = 2$  and period  $T = 1$  msec
- a. Sketch what you expect the circuit's response to the pulse train looks like
  - b. Make use of time domain arguments involving  $\tau$  to explain your graph in part (a)
  - c. Use Matlab to plot the magnitude of the envelope  $Y_{env}(f)$  as follows with a dashed line

$$|Y_{env}(f)| = |X_{env}(f)||G(jf)|$$

- d. Draw in by hand the spectral lines for  $y(t)$
- e. Compare the amplitudes of the spectral lines of  $x(t)$  and  $y(t)$
- f. Make use of your result in part (e) to explain why  $x(t)$  and  $y(t)$  look different
- g. Use Matlab to obtain the magnitudes in dBV of the first ten spectral lines of the one-sided spectral plot of  $y(t)$

## LAB

1. The objective these measurements is to see how a first order RC filter with  $a = 5\tau$  affects a 1/2 duty cycle pulse train with amplitude  $h = 2$  and period  $T = 1$  msec
  - a. Make a screen capture of the input pulse train  $x(t)$
  - b. Make a screen capture of the circuit's pulse train response  $y(t)$
  - c. Compare  $x(t)$  and  $y(t)$
  - d. Obtain and make a screen capture of the one-sided spectral plots of  $x(t)$  and  $y(t)$
  - e. Use Excel to record your measured magnitudes  $c_0 - c_{10}$  of the first ten harmonics in dBV

- of  $x(t)$  and  $y(t)$
- f. Describe and explain the differences between the spectral plots of  $x(t)$  and  $y(t)$
2. The objective of these measurements is to see how a first order RC filter with  $a = 2\tau$  affects a 1/2 duty cycle pulse train with amplitude  $h = 2$  and period  $T = 1$  msec
    - a. Make a screen capture of the input pulse train  $x(t)$
    - b. Make a screen capture of the circuit's pulse train response  $y(t)$
    - c. Compare  $x(t)$  and  $y(t)$
    - d. Obtain and make a screen capture of the one-sided spectral plot of  $y(t)$
    - e. Use Excel to record your measured magnitudes  $c_0 - c_{10}$  of the first ten harmonics in dBV of  $y(t)$
    - f. Describe and explain the differences between the spectral plots of  $x(t)$  and  $y(t)$
  3. The objective of these measurements is to see how the RC circuit of Problem (1) responds to a 1/4 duty cycle pulse train with  $h = 2$  and period  $T = 1$  msec
    - a. Make a screen capture of the input pulse train  $x(t)$
    - b. Make a screen capture of the circuit's pulse train response  $y(t)$
    - c. Compare  $x(t)$  and  $y(t)$
    - d. Obtain and make a screen capture of the one-sided spectral plot of  $y(t)$
    - e. Use Excel to record your measured magnitudes  $c_0 - c_{10}$  of the first ten harmonics in dBV of  $y(t)$
    - f. Describe and explain the differences between the spectral plots of  $x(t)$  and  $y(t)$

## POSTLAB

1. Compare your calculated and measured results for the magnitudes of the spectral lines of  $y(t)$  at the output of the RC filter in Lab Problem (1) when the input is a 1/2 duty cycle pulse train with  $a = 5\tau$ ,  $h = 2$  and period  $T = 1$  msec
2. Compare your calculated and measured results for the magnitudes of the spectral lines of  $y(t)$  at the output of the RC filter in Lab Problem (2) when the input is a 1/2 duty cycle pulse train with  $a = 2\tau$ ,  $h = 2$  and period  $T = 1$  msec
3. In Lab Problem (2) we increased  $\tau$  from  $\tau = a/5$  to  $\tau = a/2$ 
  - a. Describe how this affected the output of the filter
  - b. Use time domain arguments to explain what happened
  - c. Use frequency domain arguments to explain what happened - make use of the spectral plots of  $x(t)$  and  $y(t)$
4. Compare your calculated and measured results for the magnitudes of the spectral lines of  $y(t)$  at the output of the RC filter in Lab Problem (3) when the input is a 1/4 duty cycle pulse train with  $h = 2$  and period  $T = 1$  msec
5. In Lab Problem (3) we decreased the duty cycle of the pulse train from 1/2 to 1/4
  - a. Describe how this affected the output of the filter
  - b. Use time domain arguments to explain what happened
  - c. Use frequency domain arguments to explain what happened - make use of the spectral plots of  $x(t)$  and  $y(t)$