

Circuit Analysis in s-Domain


Electrical and Computer Engineering Department
Cal Poly Pomona

Circuit Elements in the s-Domain


The Laplace Transform of $V(t)$ and $I(t)$ are

$$V(s) = \mathcal{L}\{v(t)\} \quad I(s) = \mathcal{L}\{i(t)\}$$

A Resistor in the s Domain

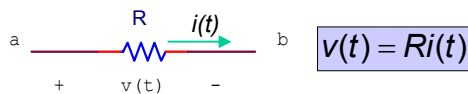


The Laplace Transform is

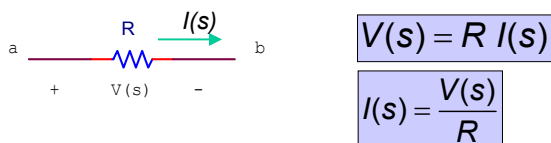

Circuit Elements in the s-Domain


An Inductor in the s Domain

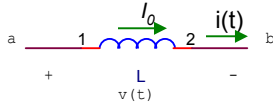


$$v(t) = L \frac{di(t)}{dt}$$

$$i(t) = \frac{1}{L} \int_{t_0}^t v(t) dt$$

The Laplace Transform is

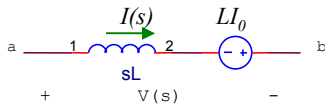
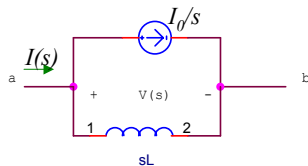
$$V(s) = L [sI(s) - i(0^-)] = LsI(s) - LI_0$$




$$I(s) = \frac{V(s) + LI_0}{sL} = \frac{1}{sL} V(s) + \frac{I_0}{s}$$

ECE 307-3 #3

Circuit Elements in the s-Domain


An capacitor in the s Domain

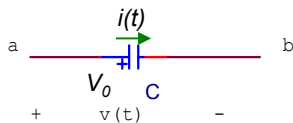


$$i(t) = C \frac{dv(t)}{dt}$$

$$v(t) = \frac{1}{C} \int_{t_0}^t i(t) dt$$

The Laplace Transform is

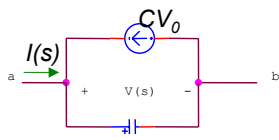
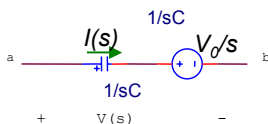
$$I(s) = C [sV(s) - v(0^-)] = CsV(s) - CV_0$$




$$V(s) = \frac{I(s) + CV_0}{sC} = \frac{1}{sC} I(s) + \frac{V_0}{s}$$

ECE 307-3 #4


Circuit Elements in the s-Domain

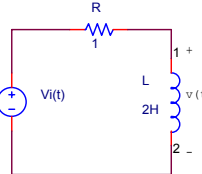Example: Calculate the voltage $v(t)$ in the following circuit.
The initial current $I_0=1A$



$3e^{-8t}u(t) \text{ V}$

The equivalent
s-domain circuit

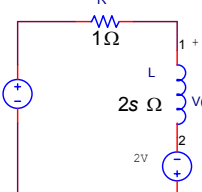

$\frac{3}{s+8} \text{ V}$

$$I(s) = \frac{3}{s+8} + 2 = \frac{s+9.5}{(s+8)(s+0.5)}$$

$$V(s) = 2s \frac{s+9.5}{(s+8)(s+0.5)} - 2$$


$$V(s) = \frac{2s-8}{(s+8)(s+0.5)}$$

$$V(s) = \frac{3.2}{(s+8)} - \frac{1.2}{(s+0.5)}$$

The result

$$v(t) = [3.2e^{-8t} - 1.2e^{-0.5t}]u(t) \text{ V}$$

Circuit Elements in the s-Domain

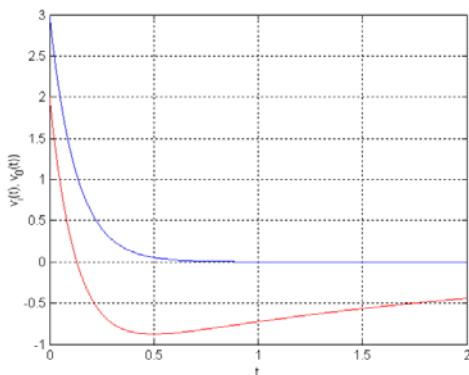


```

>> t=0:0.0001:2;
>> v=3.*exp(-8*t);
>> plot (t,v)
>> hold on
>> vo=3.2*exp(-8*t)-1.2*exp(-0.5*t);
>> plot (t,vo,'r')
>> grid on
>> xlabel ('t');
>> ylabel ('v_i(t), v_0(t)')
```

Circuit Elements in the s-Domain

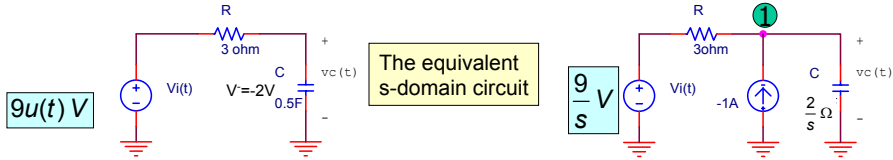Example: Calculate the voltage $v_c(t)$ in the following circuit



Write a single node (1) equation

$$-1 = \frac{V_c(s)}{2/s} + \frac{V_c(s) - 9/s}{3}$$

Solve for $V_c(s)$

$$V_c(s) = \frac{\frac{18}{s} - 6}{3s + 2} = \frac{6 - 2s}{s(s + \frac{2}{3})}$$

Partial Fraction expansion


$$V_c(s) = \frac{9}{s} - \frac{11}{s + \frac{2}{3}}$$

The result

$$v(t) = \left[9 - 11e^{-\frac{2}{3}t} \right] u(t) \text{ V}$$

ECE 307-3 #7

Circuit Elements in the s-Domain

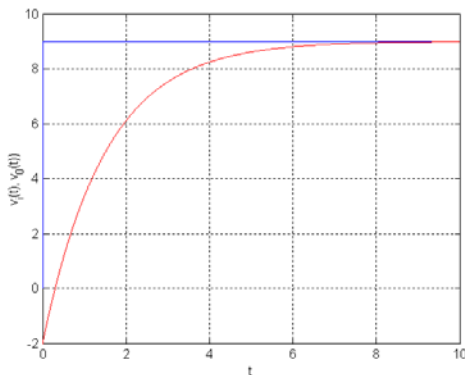


```
>> t=0:0.001:10;
>> v0=9-11*exp(-2/3*t);
>> plot (t,v0)
>> v=9*[t>0];
>> plot (t,v)
>> hold on
>> plot (t,v0, 'r')
>> xlabel ('t');
>> ylabel('v_i(t), v_0(t)')
>> grid on
```

ECE 307-3 #8

Circuit Elements in the s-Domain

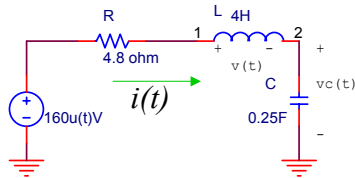Example: Find $i(t)$, Find $v(t)$ in the following circuit



Writing current ins-domain

$$I(s) = \frac{\frac{160}{s}}{4.8 + sL + \frac{1}{sC}} = \frac{160}{4s^2 + 4.8s + 4}$$

$$I(s) = \frac{40}{s^2 + 1.2s + 1}$$

Partial Fraction expansion

$$I(s) = \frac{40}{s^2 + 1.2s + 1} = \frac{-j25}{s + 0.6 - j0.8} + \frac{j25}{s + 0.6 + j0.8}$$


The result $i(t) = [50e^{-0.6t} \sin(0.8t)]u(t) \text{ A}$

Voltage in inductor

$$V(s) = \frac{160s}{(s^2 + 1.2s + 1)}$$

$$v(t) = [200e^{-0.6t} \cos(0.8t + 36.87^\circ)]u(t) \text{ V}$$


Circuit Elements in the s-Domain

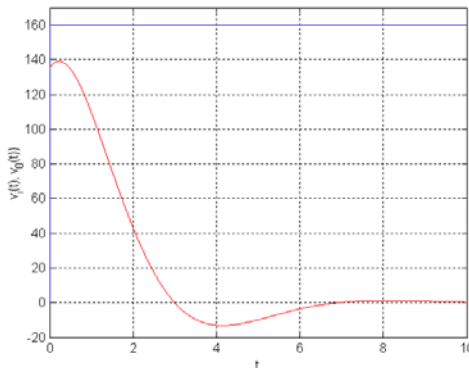

```
>> v0=200*exp(-
0.6*t).*cos(0.8*t+36.87);
>> plot(t,v0)
>> v=160*[t>0];
>> plot(t,v)
>> hold on;
>> v0=200*exp(-
0.6*t).*cos(0.8*t+36.87);
>> plot(t,v0,'r')
>> xlabel('t');
>> ylabel('v_i(t), v_0(t)');
>> grid on
>>
```

Circuit Elements in the s-Domain

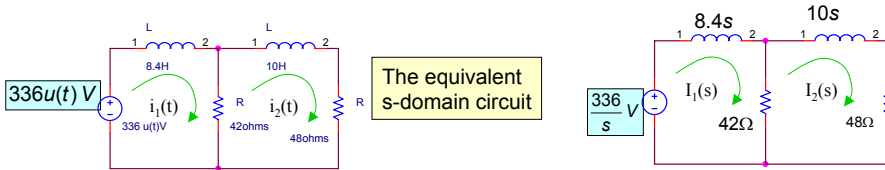Example: Calculate the voltage $v_c(t)$ in the following circuit



The equivalent s-domain circuit

The two mesh-current equations

$$\frac{336}{s} = (8.4s + 42)i_1(s) - 42i_2(s) \quad 0 = -42i_1(s) + (10s + 90)i_2(s)$$

$$\begin{bmatrix} 8.4s + 42 & -42 \\ -42 & 10s + 90 \end{bmatrix} \begin{bmatrix} I_1(s) \\ I_2(s) \end{bmatrix} = \begin{bmatrix} 336/s \\ 0 \end{bmatrix}$$

ECE 307-3 #11

Circuit Elements in the s-Domain

Example: (cont)

$$I_1(s) = \begin{bmatrix} 336/s & -42 \\ 0 & 10s + 90 \\ 8.4s + 42 & -42 \\ -42 & 10s + 90 \end{bmatrix}$$

$$I_1(s) = \frac{40(s + 9)}{s(s + 2)(s + 12)}$$

Therefore $f(t)$ can be obtain

$$i_1(t) = [15 - 14e^{-2t} - e^{-12t}]u(t) \text{ A}$$

$$I_2(s) = \begin{bmatrix} 8.4s + 42 & 336/s \\ -42 & 0 \\ 8.4s + 42 & -42 \\ -42 & 10s + 90 \end{bmatrix}$$

$$I_2(s) = \frac{168}{s(s + 2)(s + 12)}$$

The inverse transform of

$$i_2(t) = [7 - 8.4e^{-2t} + 1.4e^{-12t}]u(t) \text{ A}$$

ECE 307-3 #12

Circuit Elements in the s-Domain

MatLab To find partial fraction

$$X(s) = \frac{10s^2 + 25s}{(18s^3 + 21s^2 + 54s + 28)}$$

```
>> num = [10 25 0];  
>> den = [18 21 54 28];  
>> [r p y] = residue(num, den)
```

ECE 307-3 #13

Circuit Elements in the s-Domain

MatLab To find partial fraction

$$X(s) = \frac{5s^4}{(s^2 + 9)(90s^3 + 18s^2 + 40s + 4)}$$

```
>> d1 = 's^2+9';  
>> d2 = '90*s^3+18*s^2+40*s+4';  
>> d = symmul(d1,d2);  
>> denominator = expand(d);  
>> den=sym2poly(denominator);  
>> num = [5 0 0 0 0];  
>> [r p y] = residue(num, den)
```

ECE 307-3 #14