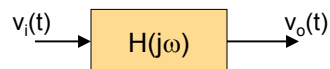


Fourier Series-II

Z. Aliyazicioglu
Electrical & Computer Engineering Dept.
Cal Poly Pomona

Fourier Series

Calculation of Steady State Responses to Periodic Inputs



Let's have sinusoidal input signal as

$$v_i(t) = V_m \cos(\omega_0 t + \theta)$$

If we know the system transfer function as $H(j\omega)$, then we can find the output as

$$v_o(t) = V_m |H(j\omega_0)| \cos[\omega_0 t + \theta \angle H(j\omega_0)]$$

t

Fourier Series

Calculation of Steady State Responses to Periodic Inputs

We know that a periodic signal $v_i(t)$ can be expressed in a Fourier Series expansion

$$v_i(t) = c_0 + \sum_{n=1}^{\infty} c_n \cos(n\omega_0 t + \theta_n)$$

We can also represent the output signal as

$$v_o(t) = c_0 |H(j0)| + \sum_{n=1}^{\infty} c_n |H(jn\omega_0)| \cos[n\omega_0 t + \theta_n + \angle H(jn\omega_0)]$$


Which is same sum of harmonic as at the input but the magnitudes and phases are changed

$$C_n |H(jn\omega_0)|$$

$$\theta_n + \angle H(jn\omega_0)$$

Fourier Series

Example:

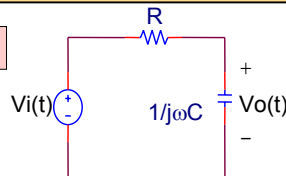

$$H(j\omega) = \frac{1}{RC} \frac{1}{j\omega + \frac{1}{RC}}$$

Magnitude Response

$$|H(j\omega)| = \frac{1}{RC} \frac{1}{\sqrt{\omega^2 + \left(\frac{1}{RC}\right)^2}}$$

Phase Response

$$\theta(j\omega) = -\tan^{-1}(\omega RC)$$

A series RC low-pass filter cutoff frequency is 8KHz. $R=10K\Omega$, $C=1.99 \text{ nF}$


$$|H(j\omega)| = \frac{(4.26)10^4}{\sqrt{\omega^2 + ((4.26)10^4)^2}}$$

Fourier Series

$$T=0.5\text{ms}$$

$$d=a/T=1/2$$
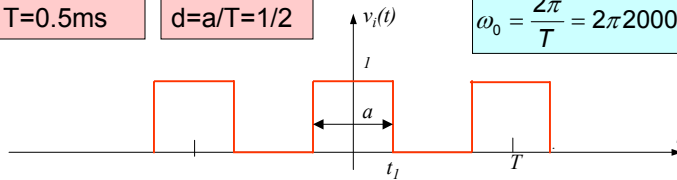
$$\omega_0 = \frac{2\pi}{T} = 2\pi 2000 \text{ rad/s}$$



$$v_i(t) = \frac{1}{2} + \frac{2}{\pi} \cos(\omega_0 t) - \frac{2}{3\pi} \cos(3\omega_0 t) + \frac{2}{5\pi} \sin(5\omega_0 t) - \frac{2}{7\pi} \cos(7\omega_0 t) \dots$$

$$|H(j0)| = 1$$

$$|H(j\omega_0)| = \frac{(4.26)10^4}{\sqrt{\omega_0^2 + ((4.26)10^4)^2}} = 0.97$$

$$\theta(j\omega_0) = -\tan^{-1}(\omega_0 RC) = -14^\circ$$

$$|H(j3\omega_0)| = 0.80$$

$$\theta(j3\omega_0) = -36.87^\circ$$

$$|H(j5\omega_0)| = 0.6246$$

$$\theta(j5\omega_0) = -51.35^\circ$$

$$|H(j7\omega_0)| = 0.496$$

$$\theta(j7\omega_0) = -60.26^\circ$$

```
>> R=10000;
>> C=1.99e-9;
>> K=1/(R*C);
>> n=1:2:7;
>> wo=2*pi*2000;
>> H=K./((j*n*wo)+K);
>> Habs=abs(H);
>> degree=angle(H)*180/pi
```

Fourier Series

The output voltage

$$v_o(t) = \frac{1}{2}(1) + \frac{2}{\pi} 0.97 \cos(\omega_0 t - 14^\circ) - \frac{2}{3\pi} 0.80 \cos(3\omega_0 t - 36.87^\circ) + \frac{2}{5\pi} 0.62 \sin(5\omega_0 t - 51^\circ) - \frac{2}{7\pi} 0.49 \cos(7\omega_0 t - 60^\circ) \dots$$

$$v_o(t) = \frac{1}{2}(1) + \frac{1.94}{\pi} \cos(\omega_0 t - 14^\circ) - \frac{1.6}{3\pi} \cos(3\omega_0 t - 36.87^\circ) + \frac{1.24}{5\pi} \sin(5\omega_0 t - 51^\circ) - \frac{0.98}{7\pi} \cos(7\omega_0 t - 60^\circ) \dots$$


$$C_n |H(jn\omega_0)|$$

```
>> cn=2./(n*pi).*Habs
```

```
cn = 0.6176    0.1697    0.0795    0.0451
```



Fourier Series

Example:

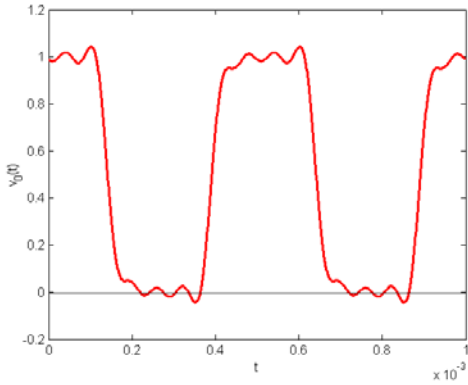

```
>> R=10000;
>> C=1.99e-9;
>> K=1/(R*C);
>> n=1:2:7;
>> wo=2*pi*2000;
>> H=K./((j*n*wo)+K);
>> Habs=abs(H)
>> degree=angle(H)*180/pi
>> cn=2./(n*pi).*Habs
cn =    0.6176    0.1697
      0.0795    0.0451
>> t=0:0.000001:0.001;
>> c1=0.6176*cos(2*pi*2000*t-
14*pi/180);
>>
c3=0.1697*cos(2*pi*3*2000*t-
36.87*pi/180);
>>
c5=0.0795*cos(2*pi*5*2000*t-
51.35*pi/180);
>>
c7=0.0451*cos(2*pi*7*2000*t-
60.26*pi/180);
>> c=c0.5+c1-c3+c5-c7;
>> plot(t,c)
>> xlabel('t')
>> ylabel('v_0(t)')
```

Fourier Series

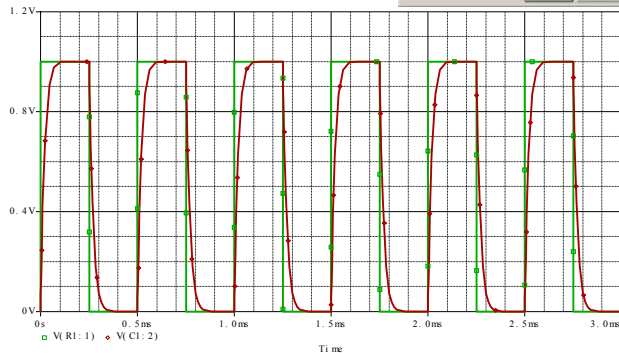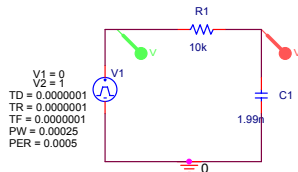

Fourier Series

Calculation of Steady State Responses to Periodic Inputs expressed as sum of Complex Exponential

$$x(t) = c_0 + \sum_{n=1}^{\infty} c_n \cos(n\omega_0 t + \theta_n) = \sum_{n=-\infty}^{\infty} X_n e^{jn\omega_0 t}$$

We can also represent the output signal as


$$v_o(t) = \sum_{n=-\infty}^{\infty} X_n H(jn\omega_0) e^{jn\omega_0 t}$$

Remember that

$$H(-j\omega) = H^*(j\omega)$$

Fourier Series

Example:

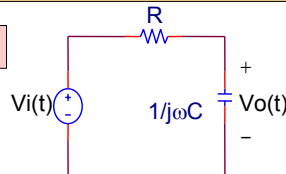

Transfer function

$$H(j\omega) = \frac{1}{1 + j\omega RC}$$


A series RC low-pass filter cutoff frequency is $R=1\text{K}\Omega$, $C=1\ \mu\text{F}$

$$H(j\omega) = \frac{1}{1 + j\omega 10^{-3}}$$

$$T=1\text{ms}$$

$$d=a/T=1/2$$
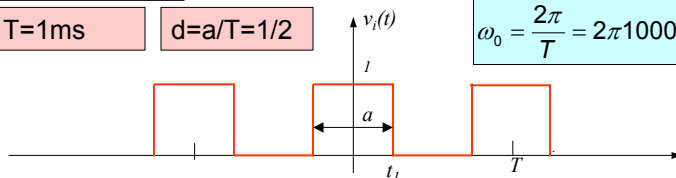
$$\omega_0 = \frac{2\pi}{T} = 2\pi 1000 \text{ rad/s}$$



$$v_i(t) = \sum_{n=-\infty}^{\infty} X_n e^{jn\omega_0 t} = \sum_{n=-\infty}^{\infty} \frac{1}{2} \text{sinc}\left(\frac{n}{2}\right) e^{jn\omega_0 t}$$

Fourier Series

The output is

$$v_0(t) = \sum_{n=-\infty}^{\infty} X_n H(jn\omega_0) e^{jn\omega_0 t} = \sum_{n=-\infty}^{\infty} \frac{\frac{1}{2} \operatorname{sinc}\left(\frac{n}{2}\right)}{1 + jn\omega_0 10^{-3}} e^{jn\omega_0 t}$$

$$v_0(t) = \sum_{n=-\infty}^{\infty} \frac{\frac{1}{2} \operatorname{sinc}\left(\frac{n}{2}\right)}{1 + jn2\pi} e^{jn\omega_0 t}$$


$$v_0(t) = \frac{1}{2} + \frac{0.3183}{1 + j2\pi} e^{j\omega_0 t} + \frac{0.3183}{1 - j2\pi} e^{-j\omega_0 t} - \frac{0.1061}{1 + j6\pi} e^{j3\omega_0 t} - \frac{0.3183}{1 - j6\pi} e^{-j3\omega_0 t} + \frac{0.0637}{1 + j10\pi} e^{j5\omega_0 t} - \frac{0.0637}{1 - j10\pi} e^{-j5\omega_0 t}$$

$$v_0(t) = \frac{1}{2} + 0.05e^{-j81^\circ} e^{j\omega_0 t} + 0.05e^{+j81^\circ} e^{-j\omega_0 t} - 0.0056e^{-j93^\circ} e^{j3\omega_0 t} - 0.0056e^{+j93^\circ} e^{-j3\omega_0 t} + 0.002e^{j88^\circ} e^{j5\omega_0 t} - 0.002e^{-j88^\circ} e^{-j5\omega_0 t}$$

$$v_0(t) = \frac{1}{2} + 0.1\cos(\omega_0 t - 81^\circ) - 0.0112\cos(3\omega_0 t - 93^\circ) + 0.004\cos(5\omega_0 t - 88^\circ)$$

Fourier Series

MatLab

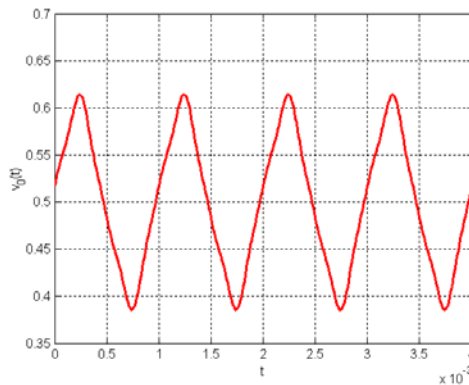

```
>> t=0:0.00001:0.004;
>> wo=2*pi*1000;
>> y1=0.1*cos(wo*t-81*pi/180);
>> y3=0.0112*cos(3*wo*t-93*pi/180);
>> y5=0.004*cos(5*wo*t-88*pi/180);
>> y=0.5+y1-y3+y5;
>> plot(t,y)
>> grid on
>> xlabel('t')
>> ylabel('v_0(t)')
```

Fourier Series

PSpice

