

Frequency Response of a Circuit

Z. Aliyazicioglu

Electrical and Computer Engineering Department
Cal Poly Pomona

Frequency Response of a Circuit

Some Preliminaries

Analysis of a circuit with varying frequency of a sinusoidal sources is called the **frequency response** of a circuit

Frequency selection in the circuits are called filters because of their ability to filter out certain input signals on the basis of frequency



Frequency Response of a Circuit

Some Preliminaries

We remember that the transfer function is the output voltage to the input voltage of a circuit in s-domain is.

$$H(s) = \frac{V_o(s)}{V_i(s)}$$

Using sinusoidal source, the transfer function will be the **magnitude** and **phase** of output voltage to the magnitude and phase of input voltage of a circuit .

In this case we will use $(j\omega)$ instead of s .

$$H(j\omega) = \frac{V_o(j\omega)}{V_i(j\omega)}$$

ECE 307-4 3



Frequency Response of a Circuit

Frequency Response

Using transfer function of circuit, we plot a frequency response of the circuit for both **amplitude** and **phase** with changing source frequency

One graph of $|H(j\omega)|$ versus frequency $j\omega$. It is called the **Magnitude plot**.

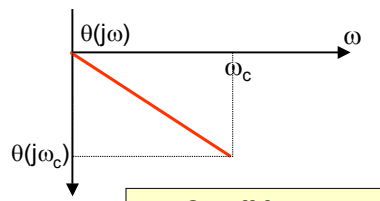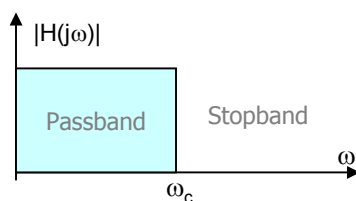One graph of $\theta(j\omega)$ versus frequency ω . It is called the **Phase Angle plot**



ω_c : Cutoff frequency


ECE 307-4 4

Frequency Response of a Circuit


Filter

A **Low-Pass filter** passes signals at frequencies lower than the cutoff frequency from the input to the output

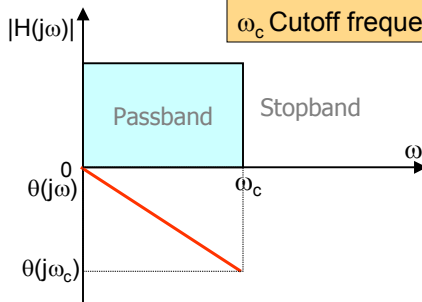A **High-Pass filter** passes signals at frequencies higher than the cutoff frequency from the input to the output



Ideal Low-Pass Filter

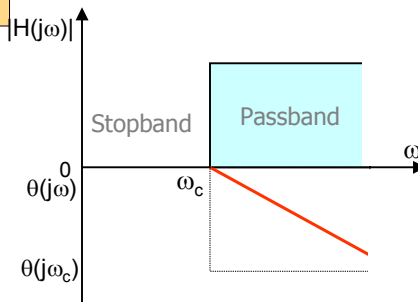

Ideal High-Pass Filter


ECE 307-4 5

Frequency Response of a Circuit


Filter

A **Band-Pass filter** passes signals within the band defined by two cutoff frequencies from the input to the output

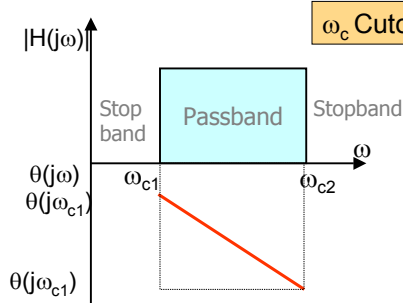A **Band-reject filter** passes signals outside the band defined by two cutoff frequencies from the input to the output



Ideal Band-Pass Filter

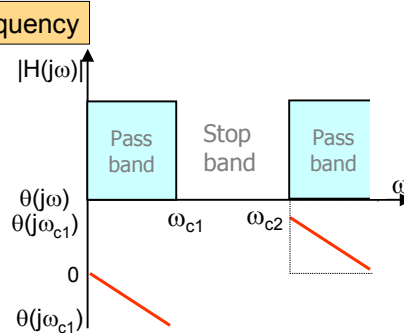

Ideal Band-Reject Filter

ECE 307-4 6

Frequency Response of a Circuit

Cutoff Frequency

The transfer function magnitude is decreased by the factor $1/\sqrt{2}$ from its maximum value is called **cutoff frequency**

$$|H(j\omega_c)| = \frac{1}{\sqrt{2}} |H_{\max}|$$


$|H_{\max}|$ is the maximum magnitude of the transfer function

ECE 307-4 7

Frequency Response of a Circuit

Low-Pass Filter

A Serial RL Circuit

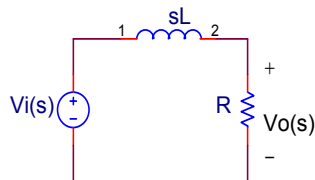

$$\frac{V_o(s)}{V_i(s)} = \frac{R}{sL + R}$$

$$H(s) = \frac{\frac{R}{L}}{s + \frac{R}{L}}$$

To find frequency response, substitute $s=j\omega$ in equation

$$H(j\omega) = \frac{\frac{R}{L}}{j\omega + \frac{R}{L}}$$

Magnitude Response

$$|H(j\omega)| = \frac{\frac{R}{L}}{\sqrt{\omega^2 + \left(\frac{R}{L}\right)^2}}$$

Phase Response

$$\theta(j\omega) = -\tan^{-1}\left(\frac{\omega L}{R}\right)$$

ECE 307-4 8

Frequency Response of a Circuit

A Serial RL Circuit

When $\omega=0$

$$|H(j0)| = \frac{\frac{R}{L}}{\sqrt{0^2 + \left(\frac{R}{L}\right)^2}} = 1$$

$$\theta(j0) = -\tan^{-1}\left(\frac{0L}{R}\right) = 0^\circ$$

When $\omega=\infty$

$$|H(j\infty)| = \frac{\frac{R}{L}}{\sqrt{\infty^2 + \left(\frac{R}{L}\right)^2}} = 0$$

$$\theta(j\infty) = -\tan^{-1}\left(\frac{\infty L}{R}\right) = -90^\circ$$

To find Cutoff Frequency

$$|H(j\omega_c)| = \frac{\frac{R}{L}}{\sqrt{\omega_c^2 + \left(\frac{R}{L}\right)^2}} = \frac{1}{\sqrt{2}}$$

Result

$$\omega_c = \frac{R}{L}$$

ECE 307-4 9


Frequency Response of a Circuit

Example

$R=1K\Omega$ $F=1KHz$. $L=?$ Plot $H(j\omega)$.

$$L = \frac{R}{\omega_c} = \frac{1000}{2 * \pi * 1000} = 0.159 H$$
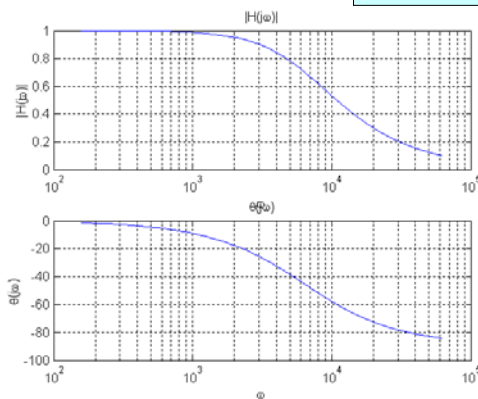
$$H(j\omega) = \frac{1000}{j\omega + \frac{1000}{0.159}}$$




```
>> R=1000;
>> L=0.159;
>> f=0.25:10000;
>> w=2*pi*f;
>> subplot (2,1,1)
>> h=abs((R/L)./(j*w+(R/L)));
>> semilogx(w,h)
>> grid on
>> title('|H(j\omega)|')
>> xlabel ('\omega')
>> ylabel ('|H(j\omega)|')
>> theta=angle((R/L)./(j*w+(R/L)));
>> subplot (2,1,2)
>> degree=theta*180/pi;
>> semilogx(w,degree)
>> grid on
>> title('\theta(j\omega)')
>> xlabel ('\omega')
>> ylabel ('\theta(j\omega)')
```

Frequency Response of a Circuit

Example

$R=1K\Omega$ $F=1KHz$. $L=?$ Plot $H(j\omega)$.

$$H(s) = \frac{R/L}{s + R/L}$$

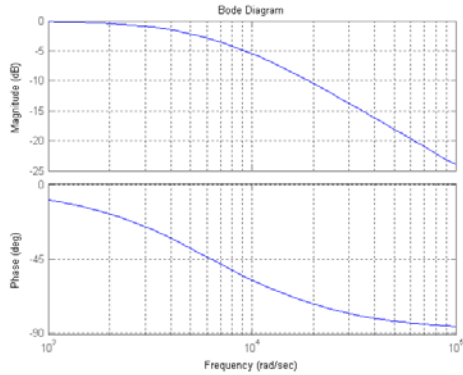

Matlab

```
>> syms s
>> n=[0 1000/0.159];
>> d=[1 1000/0.159];
>> g=tf(n,d)
```

Transfer function:




6289

s + 6289

```
>> bode (g)
>> grid on
```

Frequency Response of a Circuit


Example

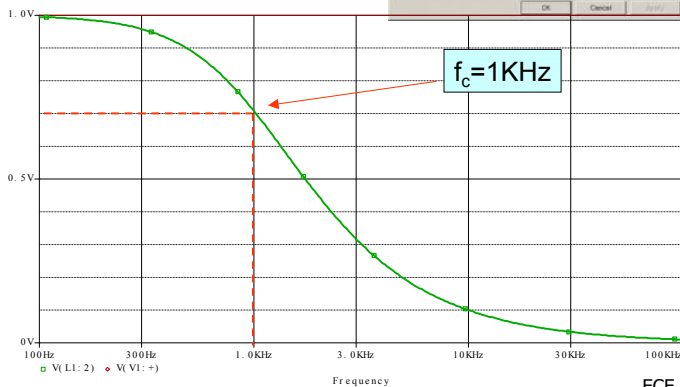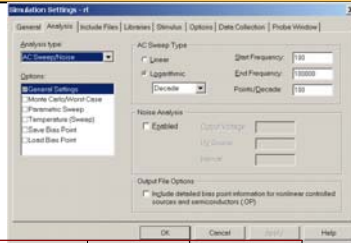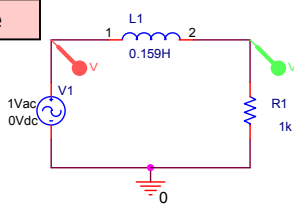

Frequency Response of a Circuit

Low-Pass Filter

A Serial RC Circuit

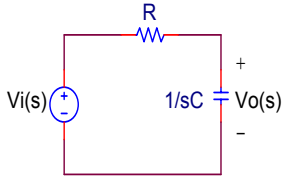

$$\frac{V_o(s)}{V_i(s)} = \frac{\frac{1}{sC}}{R + \frac{1}{sC}}$$

$$H(s) = \frac{\frac{1}{RC}}{s + \frac{1}{RC}}$$

To find frequency response, substitute $s=j\omega$ in equation

$$H(j\omega) = \frac{\frac{1}{RC}}{j\omega + \frac{1}{RC}}$$

Magnitude Response

$$|H(j\omega)| = \frac{\frac{1}{RC}}{\sqrt{\omega^2 + \left(\frac{1}{RC}\right)^2}}$$

Phase Response

$$\theta(j\omega) = -\tan^{-1}(\omega RC)$$

ECE 307-4 13

Frequency Response of a Circuit

A Serial RC Circuit

When $\omega=0$

$$|H(j0)| = \frac{\frac{1}{RC}}{\sqrt{0^2 + \left(\frac{1}{RC}\right)^2}} = 1$$

$$\theta(j0) = -\tan^{-1}(0RC) = 0^\circ$$

When $\omega=\infty$

$$|H(j\infty)| = \frac{\frac{1}{RC}}{\sqrt{\infty^2 + \left(\frac{1}{RC}\right)^2}} = 0$$

$$\theta(j\infty) = -\tan^{-1}(\infty RC) = -90^\circ$$

To find Cutoff Frequency

$$|H(j\omega_c)| = \frac{\frac{1}{RC}}{\sqrt{\omega_c^2 + \left(\frac{1}{RC}\right)^2}} = \frac{1}{\sqrt{2}}$$

Result

$$\omega_c = \frac{1}{RC}$$

ECE 307-4 14

Frequency Response of a Circuit

Example A series RC low-pass filter cutoff frequency is 8KHz.
R=10KΩ Find the capacitor value

$$\omega_c = \frac{1}{RC}$$

$$C = \frac{1}{\omega_c R}$$

$$C = \frac{1}{2 * \pi * 8000 * 10000} = 1.99 \text{ nF}$$

Example A series RL low-pass filter cutoff frequency is 2KHz.
R=5KΩ Find the inductor value. Find |H(jω)| at 50 KHz?

$$\omega_c = \frac{R}{L}$$

$$L = \frac{R}{\omega_c}$$


$$L = \frac{5000}{2000} = 2.5 \text{ H}$$

$$|H(j\omega)|_{50\text{KHz}} = \frac{R}{\sqrt{\omega^2 + \left(\frac{R}{L}\right)^2}} = \frac{5000}{\sqrt{(2 * \pi * 50000)^2 + \left(\frac{5000}{2.5}\right)^2}} = 0.0635$$

ECE 307-4 15

Frequency Response of a Circuit

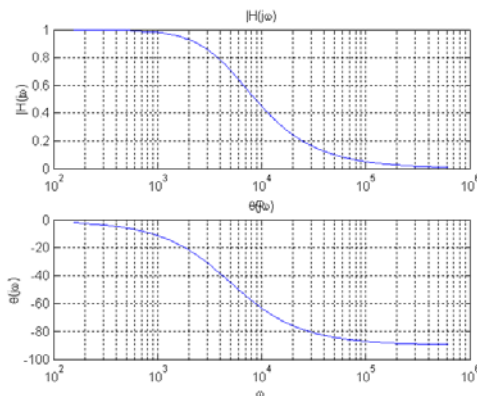Example A series RC low-pass filter cutoff frequency is 8KHz.
R=10KΩ, C=1.99 nF



```




r=10000;
c=19.9*10^-9;

f=0:25:100000;
w=2*pi*f;
h=abs(1/(r*c))./(j*w+1/(r*c));
subplot(2,1,1)
semilogx(w,h)
grid on
title('|H(j\omega)')
xlabel('\omega')
ylabel('|H(j\omega)')
theta=angle(1/(r*c))./(j*w+1/(r*c));
subplot(2,1,2)
degree=theta*180/pi;
semilogx(w,degree)
grid on
title('\theta(j\omega)')
xlabel('\omega')
ylabel('\theta(j\omega)')
    
```

ECE 307-4 16

Frequency Response of a Circuit

Example

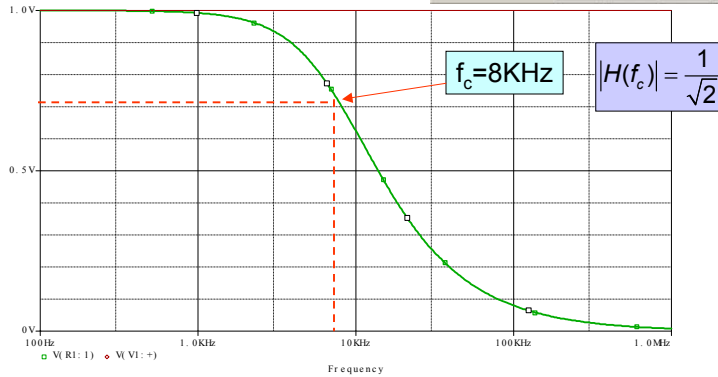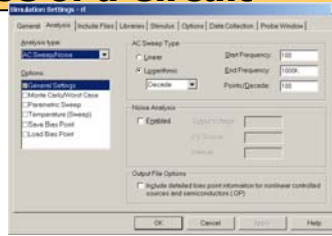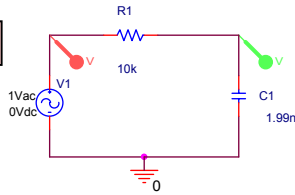


ECE 307-4 17

Frequency Response of a Circuit

High-Pass Filter

A Serial RC Circuit

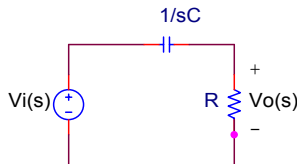

$$\frac{V_o(s)}{V_i(s)} = \frac{R}{R + \frac{1}{sC}}$$

$$H(s) = \frac{s}{s + \frac{1}{RC}}$$

To find frequency response, substitute $s=j\omega$ in equation

$$H(j\omega) = \frac{j\omega}{j\omega + \frac{1}{RC}}$$

Magnitude Response

$$|H(j\omega)| = \frac{\omega}{\sqrt{\omega^2 + \left(\frac{1}{RC}\right)^2}}$$

Phase Response

$$\theta(j\omega) = 90^\circ - \tan^{-1}(\omega RC)$$

ECE 307-4 18

Frequency Response of a Circuit

A Serial RC Circuit

When $\omega=0$

$$|H(j0)| = \frac{0}{\sqrt{0^2 + \left(\frac{1}{RC}\right)^2}} = 0$$

$$\theta(j0) = 90^\circ - \tan^{-1}\left(\frac{0}{RC}\right) = 90^\circ$$

When $\omega=\infty$

$$|H(j\infty)| = \frac{\infty}{\sqrt{\infty^2 + \left(\frac{1}{RC}\right)^2}} = 1$$

$$\theta(j\infty) = 90^\circ - \tan^{-1}\left(\frac{\infty}{RC}\right) = 0^\circ$$

To find Cutoff Frequency

$$|H(j\omega_c)| = \frac{\omega_c}{\sqrt{\omega_c^2 + \left(\frac{1}{RC}\right)^2}} = \frac{1}{\sqrt{2}}$$

Result


$$\omega_c = \frac{1}{RC}$$

ECE 307-4 19

Frequency Response of a Circuit

High-Pass Filter

A Serial RL Circuit

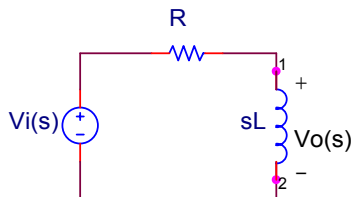

$$\frac{V_o(s)}{V_i(s)} = \frac{sL}{sL + R}$$

$$H(s) = \frac{s}{s + \frac{R}{L}}$$

To find frequency response, substitute $s=j\omega$ in equation

$$H(j\omega) = \frac{j\omega}{j\omega + \frac{R}{L}}$$

Magnitude Response

$$|H(j\omega)| = \frac{\omega}{\sqrt{\omega^2 + \left(\frac{R}{L}\right)^2}}$$

Phase Response

$$\theta(j\omega) = 90^\circ - \tan^{-1}\left(\frac{\omega L}{R}\right)$$

ECE 307-4 20

Frequency Response of a Circuit

A Serial RL Circuit

When $\omega=0$

$$|H(j0)| = \frac{0}{\sqrt{0^2 + \left(\frac{R}{L}\right)^2}} = 0$$

$$\theta(j0) = 90^\circ - \tan^{-1}\left(\frac{0L}{R}\right) = 90^\circ$$

When $\omega=\infty$

$$|H(j\infty)| = \frac{\infty}{\sqrt{\infty^2 + \left(\frac{R}{L}\right)^2}} = 1$$

$$\theta(j\infty) = 90^\circ - \tan^{-1}\left(\frac{\infty L}{R}\right) = 0^\circ$$

To find Cutoff Frequency

$$|H(j\omega_c)| = \frac{\omega_c}{\sqrt{\omega_c^2 + \left(\frac{R}{L}\right)^2}} = \frac{1}{\sqrt{2}}$$

Result

$$\omega_c = \frac{R}{L}$$

ECE 307-4 21

Frequency Response of a Circuit

Example Define R and L values for a high pass filter with a cutoff frequency of 10KHz. Find $|H(j\omega)|$ at 5 KHz

$$\omega_c = \frac{R}{L}$$

We can't calculate R and L values independently. We can select R or L values then define the other

Let $R = 1K\Omega$

$$L = \frac{R}{\omega_c}$$

Result

$$L = \frac{1000}{2 * \pi * 10000} = 15.9 \text{ mH}$$


$$|H(j\omega)|_{5\text{KHz}} = \frac{\omega}{\sqrt{\omega^2 + \left(\frac{R}{L}\right)^2}} = \frac{2 * \pi * 5000}{\sqrt{(2 * \pi * 5000)^2 + \left(\frac{1000}{0.0159}\right)^2}} = 0.4469$$

ECE 307-4 22

Frequency Response of a Circuit

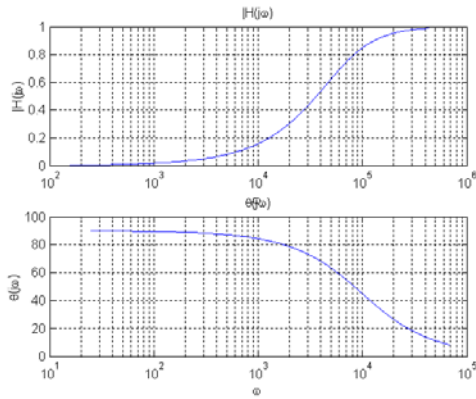Example A RL high pass filter with a cutoff frequency of 10KHz. $R = 1K\Omega$

$$L = \frac{1000}{2 * \pi * 10000} = 15.9mH$$






```
R=1000;
L=15.9*10^-3;

f=0:25:70000;
w=2*pi*f;
h=abs((j*w)./(j*w+R/L));
subplot(2,1,1)
semilogx(w,h)
grid on
title('|H(j\omega)|')
xlabel('\omega')
ylabel('|H(j\omega)|')
theta=angle((j*w)./(j*w+R/L));
subplot(2,1,2)
plot(w,theta)
degree=theta*180/pi;
semilogx(f,degree)
grid on
title('\theta(j\omega)')
xlabel('\omega')
ylabel('\theta(j\omega)')
```

ECE 307-4 23

Frequency Response of a Circuit


Example

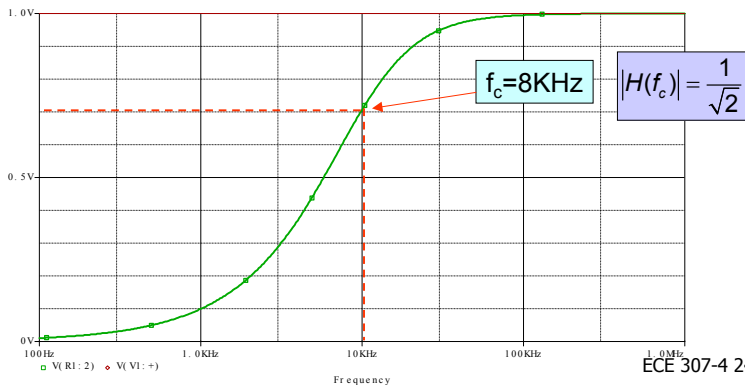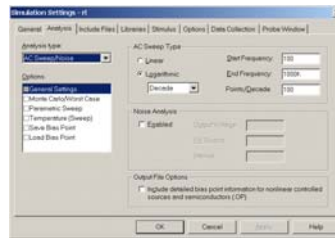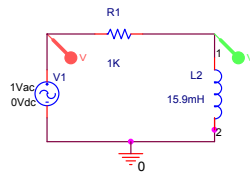


ECE 307-4 24

Frequency Response of a Circuit

Plotting phase:

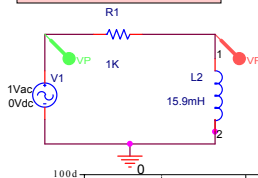

Take the probe Phase of Voltage, which is under Pspice, Markers, and Advanced.
Marked the node you want to see phase

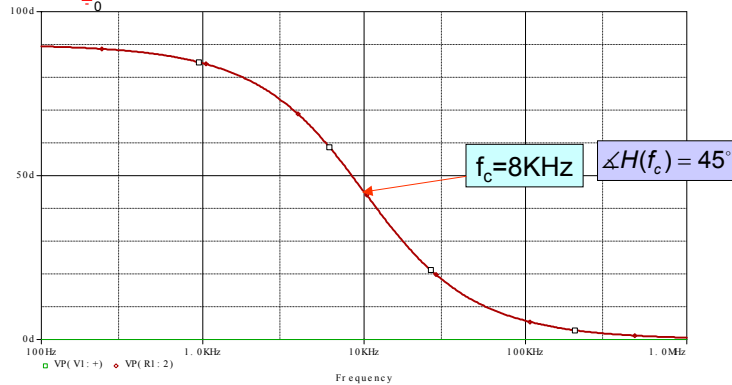


ECE 307-4 25

Frequency Response of a Circuit

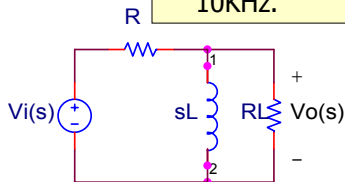Example

Let's place load resistor in parallel to inductor in RL high-pass filter shown in the figure
a. Find the transfer function
b. $R_s = R_L = 1\text{K}\Omega$, find L value for cutoff frequency at 10KHz.



$$\frac{V_o(s)}{V_i(s)} = \frac{R_L sL}{R_L + sL} \cdot \frac{R_L sL}{R + \frac{R_L sL}{R_L + sL}}$$

$$H(s) = \frac{\frac{R_L}{R + R_L} s}{s + \frac{R_L}{R + R_L} \frac{R}{L}} = \frac{Ks}{s + K \frac{R}{L}}$$

where

$$K = \frac{R_L}{R + R_L}$$

$$K = \frac{1}{1+1} = 0.5$$

Result

$$L = K \frac{R}{\omega_c} = 0.5 \frac{1}{2 * \pi * 10} = 7.95 \text{ mH}$$

$$\omega_c = K \frac{R}{L}$$


7-4 26

Frequency Response of a Circuit

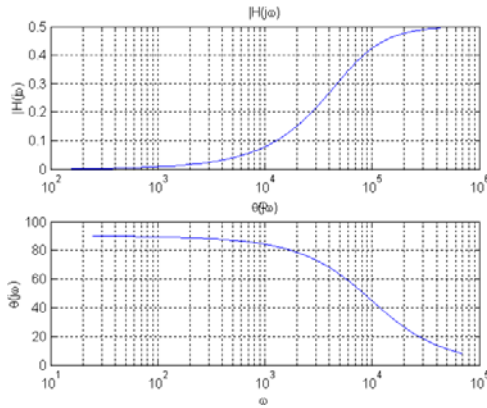Example

$R_s=R_L=1\text{K}\Omega$, $L=7.95\text{ mH}$ High-pass filter cutoff frequency at 10KHz.

$$H(j\omega) = \frac{j\omega K}{j\omega + K\frac{R}{L}}$$



```
R=1000;
RL=1000;
L=7.95*10^-3;
K=RL/(R+RL)

f=0:25:70000;
w=2*pi*f;
h=abs((j*w*K)./(j*w+K*R/L));
subplot(2,1,1)
semilogx(w,h)
grid on
title('|H(j\omega)|')
xlabel('\omega')
ylabel('|H(j\omega)|')
theta=angle((j*w*K)./(j*w+K*R/L));
subplot(2,1,2)
plot(w,theta)
degree=theta*180/pi;
semilogx(f,degree)
grid on
title('\theta(j\omega)')
xlabel('\omega')
ylabel('\theta(j\omega)')
grid on
```

ECE 307-4 27