

## Frequency Response of a Circuit

### Band-Pass Filter

Z. Aliyazicioglu

Electrical and Computer Engineering Department  
Cal Poly Pomona

## Frequency Response of a Circuit

### Band-Pass Filter

Three important parameters

**Center frequency** (or **resonance frequency**),  $\omega_0$  is defined as the frequency for which the transfer function of a circuit is purely real

$$\omega_0 = \sqrt{\omega_{c1}\omega_{c2}}$$

**Bandwidth**,  $\beta$  is the width of the passband

$$\beta = \omega_{c2} - \omega_{c1}$$

$$\beta = f_{c2} - f_{c1}$$

**Quality factor** is the ration of the center frequency  $\omega_0$  to the bandwidth  $\beta$ .

$$Q = \frac{\omega_0}{\omega_{c2} - \omega_{c1}}$$


$$Q = \frac{\omega_0}{\beta}$$

$$Q = \frac{f_0}{f_{c2} - f_{c1}}$$

## Frequency Response of a Circuit

### Band-Pass Filter

### A Serial RLC Circuit

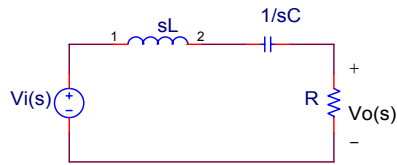

$$\frac{V_o(s)}{V_i(s)} = \frac{R}{sL + R + \frac{1}{sC}}$$

$$H(s) = \frac{\frac{R}{L}s}{s^2 + \frac{R}{L}s + \frac{1}{LC}}$$

To find frequency response, substitute  $s=j\omega$  in equation

$$H(j\omega) = \frac{\frac{R}{L}j\omega}{-\omega^2 + \frac{R}{L}j\omega + \frac{1}{LC}}$$

Magnitude Response

Phase Response

$$|H(j\omega)| = \frac{\frac{R}{L}\omega}{\sqrt{\left(\frac{1}{LC} - \omega^2\right)^2 + \left(\frac{R}{L}\omega\right)^2}}$$

$$\theta(j\omega) = 90^\circ - \tan^{-1}\left(\frac{\frac{R}{L}\omega}{\frac{1}{LC} - \omega^2}\right)$$

ECE 307-5 3

## Frequency Response of a Circuit

### A Serial RLC Circuit

At resonance frequency, the transfer function will be real.  
Or system total impedance will be real

$$j\omega_0 L + \frac{1}{j\omega_0 C} = 0$$

$$\omega_0 = \sqrt{\frac{1}{LC}}$$

$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$

$H_{\max}$  will be at  $|H(j\omega_0)|$

substitute  $\omega_0 = \sqrt{1/LC}$

$$|H(j\omega_0)| = \frac{\frac{R}{L}\omega_0}{\sqrt{\left(\frac{1}{LC} - \omega_0^2\right)^2 + \left(\frac{R}{L}\omega_0\right)^2}}$$

Result

$$|H(j\omega_0)| = \frac{\frac{R}{L}\sqrt{\frac{1}{LC}}}{\sqrt{\left(\frac{1}{LC} - \frac{1}{LC}\right)^2 + \left(\frac{R}{L}\sqrt{\frac{1}{LC}}\right)^2}} = 1$$

ECE 307-5 4

## Frequency Response of a Circuit

### A Serial RLC Circuit

Set  $(1/\sqrt{2})H_{\max}$  to find cutoff frequencies

$$\frac{1}{\sqrt{2}} = \frac{\frac{R}{L}\omega_c}{\sqrt{\left(\frac{1}{LC} - \omega_c^2\right)^2 + \left(\frac{R}{L}\omega_c\right)^2}}$$

$$\frac{1}{2} \left[ \left( \frac{1}{LC} - \omega_c^2 \right)^2 + \left( \frac{R}{L}\omega_c \right)^2 \right] = \left( \frac{R}{L}\omega_c \right)^2$$

$$\left( \frac{1}{LC} - \omega_c^2 \right)^2 = 2 \left( \frac{R}{L}\omega_c \right)^2 - \left( \frac{R}{L}\omega_c \right)^2$$

$$\left( \frac{1}{LC} - \omega_c^2 \right) = \mp \left( \frac{R}{L}\omega_c \right)$$

Result

$$\omega_c^2 + \frac{R}{L}\omega_c - \frac{1}{LC} = 0$$

$$\omega_{c1} = -\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \left(\frac{1}{LC}\right)}$$

Confirm

$$\omega_0 = \sqrt{\omega_{c1}\omega_{c2}} = \sqrt{\frac{1}{LC}}$$

$$\omega_c^2 - \frac{R}{L}\omega_c - \frac{1}{LC} = 0$$

$$\omega_{c2} = \frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \left(\frac{1}{LC}\right)}$$

ECE 307-5 5

## Frequency Response of a Circuit

### A Serial RLC Circuit

The Bandwidth  $\beta$  is

$$\begin{aligned} \beta &= \omega_{c2} - \omega_{c1} \\ &= \left[ \frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \left(\frac{1}{LC}\right)} \right] - \left[ -\frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \left(\frac{1}{LC}\right)} \right] \end{aligned}$$

$$\beta = \frac{R}{L}$$

The Quality factor Q is

$$Q = \frac{\omega_0}{\beta} = \frac{\sqrt{\frac{1}{LC}}}{\frac{R}{L}}$$

$$Q = \sqrt{\frac{L}{CR^2}}$$

$$Q = \frac{f_0}{f_{c2} - f_{c1}}$$

ECE 307-5 6

## Frequency Response of a Circuit

### A Serial RLC Circuit

The cutoff frequencies in terms of  $\beta$  and  $\omega_0$

$$\omega_{c1} = -\frac{\beta}{2} + \sqrt{\left(\frac{\beta}{2}\right)^2 + (\omega_0)^2}$$

$$\omega_{c2} = \frac{\beta}{2} + \sqrt{\left(\frac{\beta}{2}\right)^2 + (\omega_0)^2}$$

The cutoff frequencies in terms of  $Q$  and  $\omega_0$

$$\omega_{c1} = \omega_0 \left[ -\frac{1}{2Q} + \sqrt{1 + \left(\frac{1}{2Q}\right)^2} \right]$$

$$\omega_{c2} = \omega_0 \left[ \frac{1}{2Q} + \sqrt{1 + \left(\frac{1}{2Q}\right)^2} \right]$$

ECE 307-5 7

## Frequency Response of a Circuit

**Example** Using serial RLC circuit, design band pass filter that select 1-10KHz frequency band for a graphic equalizer in your amplifier

We can use different approaches. Let's find the center frequency first.

$$\omega_0 = \sqrt{\omega_{c1}\omega_{c2}} = \sqrt{\frac{1}{LC}}$$

$$f_0 = \sqrt{f_{c1}f_{c2}} = \sqrt{1000 * 10000} = 3162.28 \text{ Hz}$$

Choose capacitor value as  $1\mu\text{F}$

$$\omega_0 = \sqrt{\frac{1}{LC}} \quad L = \frac{1}{\omega_0^2 C} = \frac{1}{(2\pi 3162.28)^2 (10^{-6})} = 2.533\text{mH}$$

The Quality factor is

$$Q = \frac{f_0}{f_{c2} - f_{c1}} = \frac{3162.28}{10000 - 1000} = 0.3514$$

The Resistor is


$$Q = \sqrt{\frac{L}{CR^2}} \quad R = \sqrt{\frac{L}{CQ^2}} = \sqrt{\frac{0.00253}{10^{-6}(0.3514)^2}} = 143.24\Omega$$

ECE 307-5 8
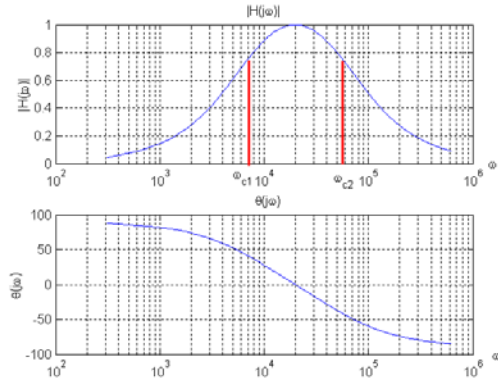
## Frequency Response of a Circuit

$R=143.25 \Omega$ ,  $L=2.533 \text{ mH}$ ,  $C=1 \mu\text{F}$ , Plot  $F=50 - 100 \text{ KHz}$ .

$$H(j\omega) = \frac{\frac{R}{L} j\omega}{-\omega^2 + \frac{R}{L} j\omega + \frac{1}{LC}}$$



```
>> R=143.25;
>> L=0.002533;
>> C=0.000001;
>> f=50:100000;
>> w=2*pi*f;
>> h=abs((R/L).*(j*w)./(-
w.^2+(R/L)*(j*w)+(1/(L*C))));
>> subplot(2,1,1)
>> semilogx(w,h)
>> grid on
>> title('|H(j\omega)|')
>> xlabel('\omega')
>> ylabel('|H(j\omega)|')
>> subplot(2,1,2)
>> theta=angle((R/L).*(j*w)./(-
w.^2+(R/L)*(j*w)+(1/(L*C))));
>> degree=theta*180/pi;
>> semilogx(w,degree)
>> grid on
>> title('theta(j\omega)')
>> xlabel('\omega')
>> ylabel('\theta(j\omega)')
```

$\omega_{c1}=6283 \text{ rad/s}$   
 $\omega_{c2}=62,831 \text{ rad/s}$



9

## Frequency Response of a Circuit

Example

OrCad Capture

Edit Simulation Profile

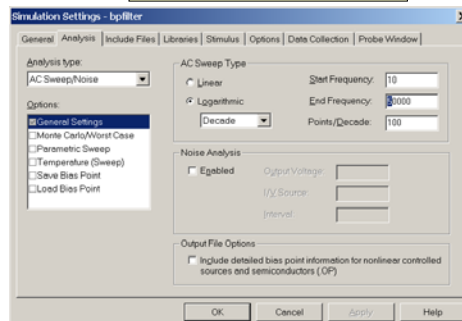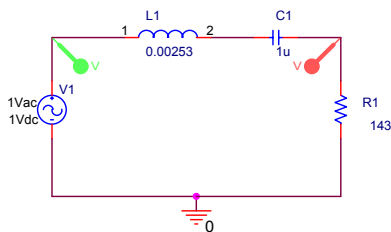

# Frequency Response of a Circuit

PSpice Result

